

# Digital System Design and Lab: HW1

Lo Chun, Chou  
R13922136

March 31, 2025

## 1

A	B	C	X	Y
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

From the values where  $X = 1$ , we can form the following equation:

$$\begin{aligned} X &= A'BC + AB'C + ABC' + ABC \\ &= m_3 + m_5 + m_6 + m_7 \\ &= \sum m(3, 5, 6, 7) \\ &= \prod M(0, 1, 2, 4) \end{aligned}$$

Similarly, from the values where  $Y = 1$ , we can form the following equation:

$$\begin{aligned} Y &= A'B'C + A'BC' + AB'C' + ABC \\ &= m_1 + m_2 + m_4 + m_7 \\ &= \sum m(1, 2, 4, 7) \\ &= \prod M(0, 3, 5, 6) \end{aligned}$$

## 2

### (1)

We form the table by first listing all possible combinations of  $A, B, C, D$  and their corresponding decimal values.

Then we calculate the decimal values multiplied by 5, and let  $S, T, U, V$  present the decimal values, and  $W, X, Y, Z$  present the values of  $0 \sim 9$  left.

A	B	C	D	decimal	decimal $\times 5$	S	T	U	V	W	X	Y	Z
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	5	0	0	0	0	0	1	0	1
0	0	1	0	2	10	0	0	0	1	0	0	0	0
0	0	1	1	3	15	0	0	0	1	0	1	0	1
0	1	0	0	4	20	0	0	1	0	0	0	0	0
0	1	0	1	5	25	0	0	1	0	0	1	0	1
0	1	1	0	6	30	0	0	1	1	0	0	0	0
0	1	1	1	7	35	0	0	1	1	0	1	0	1
1	0	0	0	8	40	0	1	0	0	0	0	0	0
1	0	0	1	9	45	0	1	0	0	0	1	0	1

### (2)

First, we can find that  $D = X = Z$ , since when  $D = 1$ , this means that the decimal value is an odd number, therefore the decimal value multiplied by 5 would have a unit digit of 5, which would result in a one in  $X$  and  $Z$ .

Then, we can find that  $C = V$ , since when  $C = 1$ , this means that the decimal value is added by 2, therefore the decimal value multiplied by 5 would result in adding a 10, which is  $V = 1$ . Similarly, we would have  $B = U$ .

Next,  $A = T$ , because when  $A = 1$ , the decimal value is greater than 8, which would result in 40 when multiplied by 5, thus the tens digit would be 4, which means  $T = 1$ .

We can observe that  $S = 0$ , since in order to have a 1 in  $S$ , the resulting value after multiplied by 5 should be greater than 80, which is impossible, because the maximum value of a BCD digit  $ABCD$  is 9.

Finally,  $W = Y = 0$ , since first, any value multiplied by 5 would not result in 2 or 8 in the unit digit, also, the maximum value of  $ABCD$  is 9, so when we have 10, it won't be  $W = Y = 1$  but moving the ten to be presented in the tens digit.

3

BC \ A		0	1
0	0	X	1
	1	1	0
1	1	0	X
	0	X	1

From the K-map, we can derive the following minimum SOP equation:

$$F(A, B, C) = A'B' + C'$$

4

(1)

First, we convert the maxterm expression into a minterm expression:

$$\begin{aligned} F(A, B, C, D) &= \prod M(0, 2, 10, 11, 12, 14, 15) \cdot \prod D(5, 7) \\ &= \sum m(1, 3, 4, 6, 8, 9, 13) \cdot \sum d(5, 7) \end{aligned}$$

Next, we draw the K-map and find the minimum SOP equation:

$CD \backslash AB$	00	01	11	10
00	0	1	0	1
01	1	<del>1</del>	1	1
11	1	<del>1</del>	0	0
10	0	1	0	0

From the K-map, we can derive the following minimum SOP equation:

$$F(A, B, C, D) = A'B + C'D + A'D + AB'C'$$

(2)

For this subproblem, we also need to convert the maxterm expression into a minterm expression first, which is the same as the previous subproblem:

$$\begin{aligned} F(A, B, C, D) &= \prod M(0, 2, 10, 11, 12, 14, 15) \cdot \prod D(5, 7) \\ &= \sum m(1, 3, 4, 6, 8, 9, 13) \cdot \sum d(5, 7) \end{aligned}$$

But in the K-map, we circle 0s instead of 1s:

$CD \backslash AB$	00	01	11	10
00	0	1	0	1
01	1	<del>1</del>	1	1
11	1	<del>1</del>	0	0
10	0	1	0	0

From the K-map, we can derive the following minimum SOP equation for  $F'$ :

$$F'(A, B, C, D) = A'B'D' + ABD' + AC$$

Then, we can derive the minimum POS equation for  $F$  by using De Morgan's law:

$$\begin{aligned} F(A, B, C, D) &= (F'(A, B, C, D))' \\ &= (A'B'D' + ABD' + AC)' \\ &= (A + B + D)(A' + B' + D)(A' + C') \end{aligned}$$

## 5

By the given restriction, we knew that  $ABCD = 1111$  and  $ABCD = 0101$  would never occur, so they are the don't care terms.

We then construct the K-map:

$CD \backslash AB$	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	1	1	0	0
10	1	0	0	1

From the K-map, we can derive the following simplified equation:

$$F(A, B, C, D) = B'D' + A'D + C'D$$


## 6

K-map using SOP (circle 1s):

AB \ CD	00	01	11	10
00	0	0	1	1
01	0	1	1	1
11	0	0	0	0
10	0	0	0	0

$F = A'B'C' + AC'D + AB'C'$  A'D → PI  
 or  
 $F = A'B'C' + BC'D + AB'C'$  BC'D → PI  
 $F = A'B'C' + \underline{ABC'D} + AB'C'$  ABC'D not PI  
(1's can be covered by BC'D or AC'D)

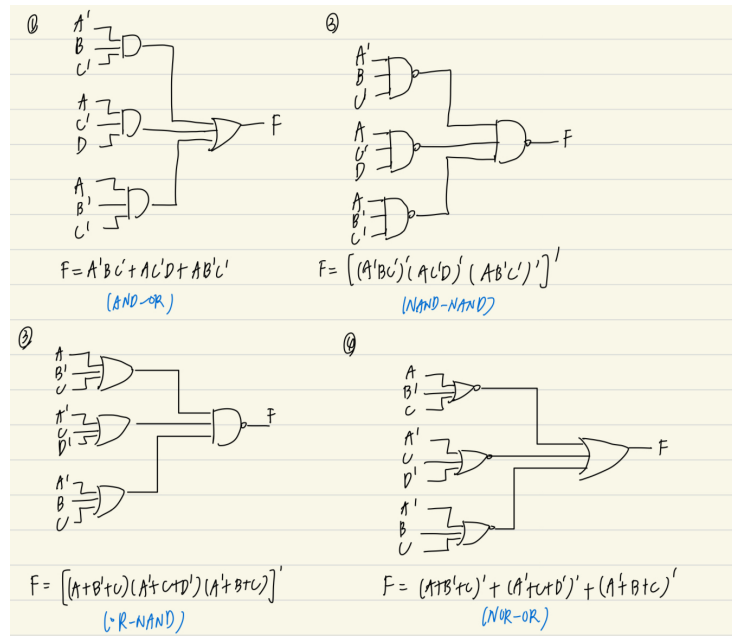From the order 1 → 2 → 3 → 4, we can formulate the first four minimum two-level gate circuits:




K-map using POS (circle 0s):

AB \ CD	00	01	11	10
00	0	1	1	1
01	0	1	1	1
11	0	0	0	0
10	0	0	0	0

$F' = A'B' + C + ABD'$   
 $\rightarrow F = (F')' = (A'B' + C + ABD')'$   
 $= (A+B)C'(A'B'+D)$

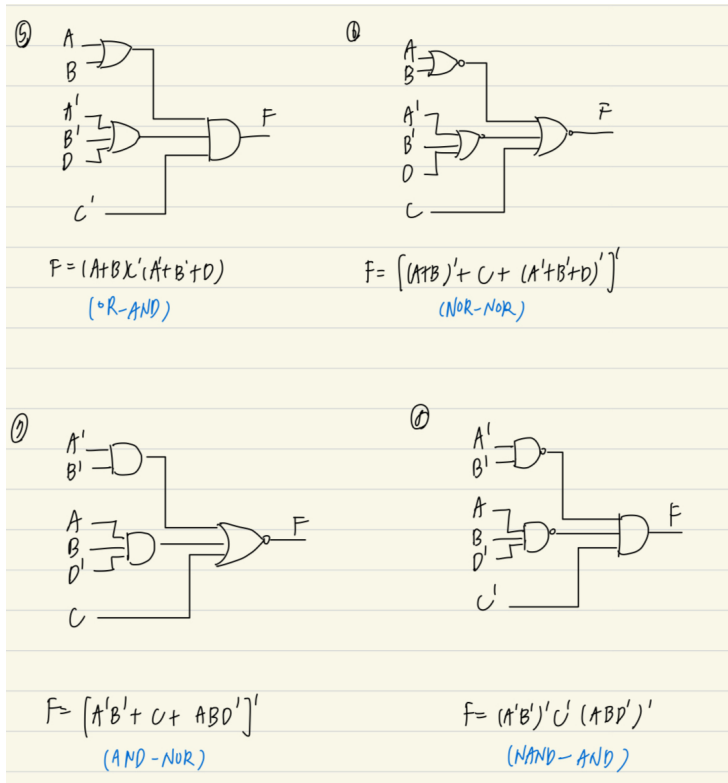From the order 5 → 6 → 7 → 8, we can formulate the first four minimum two-level gate circuits:



Since we're using K-map to ensure that both SOP / POS expressions are minimum, we can conclude that the eight two-level gate circuits are minimum.



## 7

First, we convert the maxterm expression into a minterm expression:

$$\begin{aligned} F(A, B, C, D) &= \prod M(0, 1, 3, 13, 14, 15) \\ &= \sum m(2, 4, 5, 6, 7, 8, 9, 10, 11, 12) \end{aligned}$$


Then, we draw the K-map:

	AB				
CD	00	01	11	10	
00	0	0	1	0	SOP: $F = A'B'C' + A'BD' + AC'D + AB'C'$
01	0	0	1	1	
11	1	0	0	0	
10	1	1	0	0	

	AB				
CD	00	01	11	10	
00	0	1	0	1	POS: $F' = A'B'C' + A'BD + ABD' + AC$ $\rightarrow F = (F')' = (A'B'C' + A'BD + ABD' + AC)'$ $= (A+B+C)(A+B'+D')(A+B'+D)(A'+C')$
01	0	0	1	1	
11	1	0	0	0	
10	1	1	0	0	

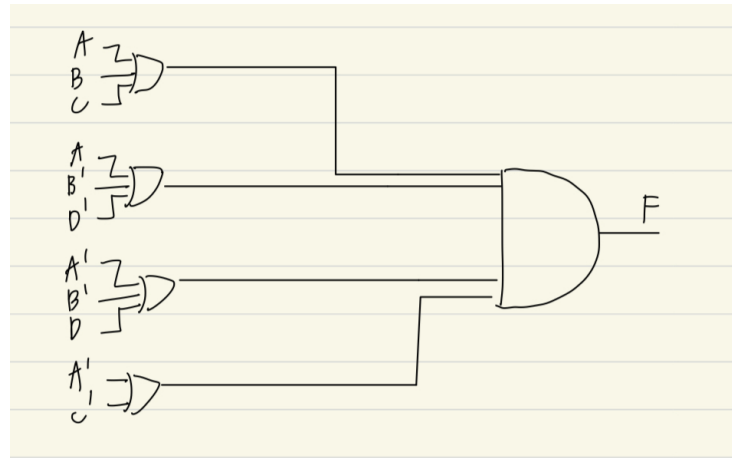From the K-map, we can formulate the circuit with only AND, OR gates:



There are 5 gates and 11 gate inputs in the circuit.