

Digital System Design and Lab: HW4

Lo Chun, Chou  
R13922136

May 18, 2025

1  
(1)

Present State			Next State		
$C$	$B$	$A$	$C^+$	$B^+$	$A^+$
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	1

 


Figure 1: K-maps

(2)

The K-maps for D flip-flop are the same as the K-maps for  $C^+$ ,  $B^+$ , and  $A^+$  in (1), since we assign the values of  $D_C$ ,  $D_B$ , and  $D_A$  to be  $C^+$ ,  $B^+$ , and  $A^+$  respectively.

Thus, the following  $D_C$  is the same as  $C^+$ :

		$C$	
		0	1
$BA$	00	X	0
	01	0	1
	11	0	1
	10	1	1

Figure 2: D flip-flop ( $D_C$ )

The minimum SOP expression for  $D_C$  is:

$$D_C = AC + A'B$$

(3)

Since  $C$  is toggled for  $CBA = \{010, 100\}$ , we can derive the following K-map for  $T_C$ :

		$C$	
		0	1
$BA$	00	X	1
	01	0	0
	11	0	0
	10	1	0

Figure 3: T flip-flop ( $T_C$ )

The minimum SOP expression for  $T_C$  is:

$$T_C = A'B' + A'C'$$

(4)

From the truth table is subproblem (1), we have:

$$\{B, B^+\} = \begin{cases} \{0, 0\} & \text{for } CBA = \{101, 100\} \rightarrow \{S, R\} = \{0, X\} \\ \{0, 1\} & \text{for } CBA = \{001\} \rightarrow \{S, R\} = \{1, 0\} \\ \{1, 0\} & \text{for } CBA = \{111\} \rightarrow \{S, R\} = \{0, 1\} \\ \{1, 1\} & \text{for } CBA = \{011, 010, 110\} \rightarrow \{S, R\} = \{X, 0\} \end{cases}$$

		<i>C</i>	
		0	1
<i>BA</i>	00	X	0
	01	1	0
	11	X	0
	10	X	X

(a)  $S_B$

		<i>C</i>	
		0	1
<i>BA</i>	00	X	X
	01	0	X
	11	0	1
	10	0	0

(b)  $R_B$

The minimum SOP expression for  $S_B, R_B$  are:

$$\begin{aligned} S_B &= C' \\ R_B &= AC \end{aligned}$$

(5)

From the truth table is subproblem (1), we have:

$$\{A, A^+\} = \begin{cases} \{0, 0\} & \text{for } CBA = \{010\} \rightarrow \{J, K\} = \{0, X\} \\ \{0, 1\} & \text{for } CBA = \{110, 100\} \rightarrow \{J, K\} = \{1, X\} \\ \{1, 0\} & \text{for } CBA = \{011, 101\} \rightarrow \{J, K\} = \{X, 1\} \\ \{1, 1\} & \text{for } CBA = \{001, 111\} \rightarrow \{J, K\} = \{X, 0\} \end{cases}$$

		<i>C</i>	
		0	1
<i>BA</i>	00	X	1
	01	X	X
	11	X	X
	10	0	1

(a)  $J_A$

		<i>C</i>	
		0	1
<i>BA</i>	00	X	X
	01	0	1
	11	1	0
	10	X	X

(b)  $K_A$

The minimum SOP expression for  $J_A, K_A$  are:

$$\begin{aligned} J_A &= C \\ K_A &= BC' + B'C \end{aligned}$$

## 2

### (1)

Following the steps to construct the state table at lecture slides 13, p. 15, we first determine the flip-flop and output equations:

$$\begin{aligned} J_1 &= X, \\ K_1 &= X \bar{\wedge} Q'_2 = (XQ'_2)' = X' + Q_2, \\ J_2 &= X, \\ K_2 &= Q_1 \bar{\wedge} X = (Q_1X)' = Q'_1 + X', \\ Z &= Q'_2 \oplus X = Q'_2X' + Q_2X \end{aligned}$$


Then, using the next state equation for JK flip-flop, which is:

$$Q^+ = JQ' + K'Q$$

we have:

$$\begin{aligned} Q_1^+ &= J_1Q'_1 + K'_1Q_1 = XQ'_1 + (X' + Q_2)'Q_1 = \underline{XQ'_1 + XQ_1Q'_2} \\ Q_2^+ &= J_2Q'_2 + K'_2Q_2 = XQ'_2 + (Q'_1 + X')'Q_2 = \underline{XQ'_2 + XQ_1Q_2} \\ Z &= \underline{Q'_2X' + Q_2X} \end{aligned}$$

 We then plot the next state map for each flip-flop:



We can then use the K-maps to form the state table:

$Q_1Q_2$	$Q_1^+Q_2^+$		$Z$	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
00	00	11	1	0
01	00	10	0	1
11	00	01	0	1
10	00	11	1	0

(2)


We first replace part of the resulting state table in subproblem (1) with the following symbols:

$$S_0 = 00, \quad S_1 = 01, \quad S_2 = 11, \quad S_3 = 10$$

Then we'll have:

$Q_1Q_2$	$Q_1^+Q_2^+$		$Z$	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
$S_0$	$S_0$	$S_2$	1	0
$S_1$	$S_0$	$S_3$	0	1
$S_2$	$S_0$	$S_1$	0	1
$S_3$	$S_0$	$S_2$	1	0

 Using this table, we can construct the state diagram:



### 3

#### (1)

From the following image, we can check that for all possible situations 0000 to 1111, what the next state should be after the input  $X = \{0, 1\}$  is applied.

Decimal digit	BCD				Next input		
	8	4	2	1	$X=1$	$X=0$	
0	0	0	0	0	0000	0000	(valid)
1	0	0	0	1	0001	0000	Green : output $Z=0$
2	0	0	1	0	0010	0001	Red : output $Z=1$
3	0	0	1	1	0011	0001	(invalid)
4	0	1	0	0	0100	0010	
5	0	1	0	1	0101	0010	
6	0	1	1	0	0110	0011	
7	0	1	1	1	0111	0011	
8	1	0	0	0	1000	0100	
9	1	0	0	1	1001	0100	
Invalid	10	1010	1101	0101			
	11	1011	1101	0101			
	12	1100	1110	0110			
	13	1101	1110	0110			
	14	1110	1111	0111			
	15	1111	1111	0111			

Let  $S_0$  be the initial state, which assumes all previous inputs were 0 as given in the problem. We then add two states  $S_1$  and  $S_2$  to represent the cases when the current input along with the previous 3 inputs is valid and invalid respectively.

This also means that the green states in the above image would go to  $S_1$  and the red states would go to  $S_2$ .

Thus, we can form the state table as follows:

Current State	Input		Z	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
$S_0$	$S_0$	$S_1$	0	0
$S_1$	$S_1$	$S_1, S_2$	0	0
$S_2$	$S_1, S_2$	$S_1, S_2$	1	1



(2)

We shall use the following four states, with each of them containing the previous 4 inputs as follows:

$$\begin{aligned} S_0 &= \{0000, 0001, 0010, 0011\} \\ S_1 &= \{0100, 0101, 0110, 0111\} \\ S_2 &= \{1000, 1001\} \\ S_3 &= \{1010, 1011, 1100, 1101, 1110, 1111\} \end{aligned}$$

For  $S_0$ , this state contains all the cases when no matter we receive any input ( $X = 0$  or  $1$ ), it would still be valid.

For  $S_1$ , this state contains the cases when it receives 0 as input, it would go to  $S_0$ , and would be invalid (go to  $S_3$ ) if it receives 1.

For  $S_2$ , this state contains the cases when it receives 0 as input, it would go to  $S_1$ , and would be invalid (go to  $S_3$ ) if it receives 1. (The distinction between  $S_1, S_2$  is that it is possible for  $S_1$  to enter the next state  $S_0$ , which would be valid no matter what next input is.)

For  $S_3$ , this state contains all the invalid cases.

We can then form the state table as follows:

Current State	Input		Z	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
$S_0$	$S_0$	$S_0$	0	0
$S_1$	$S_0$	$S_3$	0	1
$S_2$	$S_1$	$S_3$	0	1
$S_3$	$S_1$	$S_3$	0	1


4

(1)


The following screenshot is the module mult\_fast

```
1 // pipelined fast multiplier
2 module mult_fast(
3     output reg[7:0] P, // product
4     input[3:0] A, B, // multiplicand and multiplier
5     input clk // clock (posedge)
6 );
7 // stage 0 (input)
8 reg[3:0] a_s0, b_s0;
9 always @(posedge clk) begin
10     a_s0 <= A;
11     b_s0 <= B;
12 end
13 // stage 1: sum each two rows of partial products
14 wire[3:0] pp0 = a_s0 & {4{b_s0[0]}}; // ignore the delays of AND gates
15 wire[4:1] pp1 = a_s0 & {4{b_s0[1]}}; // ignore the delays of AND gates
16 wire[5:2] pp2 = a_s0 & {4{b_s0[2]}}; // ignore the delays of AND gates
17 wire[6:3] pp3 = a_s0 & {4{b_s0[3]}}; // ignore the delays of AND gates
18 reg[5:1] sum1;
19 always @(pp0, pp1)
20     sum1[5:1] <= #7 pp0[3:1] + pp1[4:1]; // delay of the 4-bit adder
21 reg[7:3] sum3;
22 always @(pp2, pp3)
23     sum3[7:3] <= #7 pp2[5:3] + pp3[6:3]; // delay of the 4-bit adder
24 reg[5:0] sum1_s1;
25 reg[7:2] sum3_s1;
26 always @(posedge clk) begin
27     sum1_s1 <= {sum1, pp0[0]};
28     sum3_s1 <= {sum3, pp2[2]};
29 end
30 // stage 2 (outout)
31 reg[7:2] sum2;
32 always @(sum1_s1, sum3_s1)
33     sum2[7:2] <= #8 sum1_s1[5:2] + sum3_s1[7:2]; // delay of the 6-bit adder
34 always @(posedge clk) begin
35     P <= {sum2, sum1_s1[1:0]};
36 end
37 endmodule
```

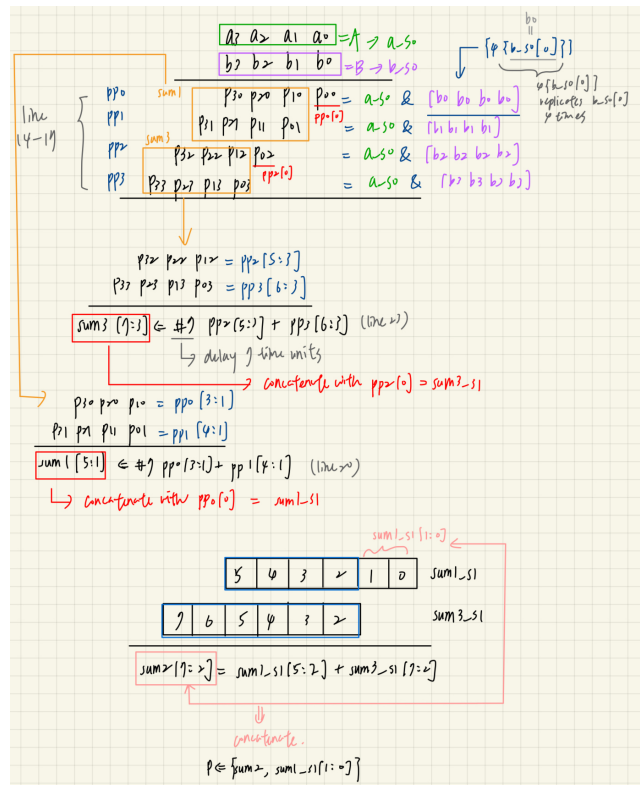And also not required, the following figure shows how the indices are decided:



(2)

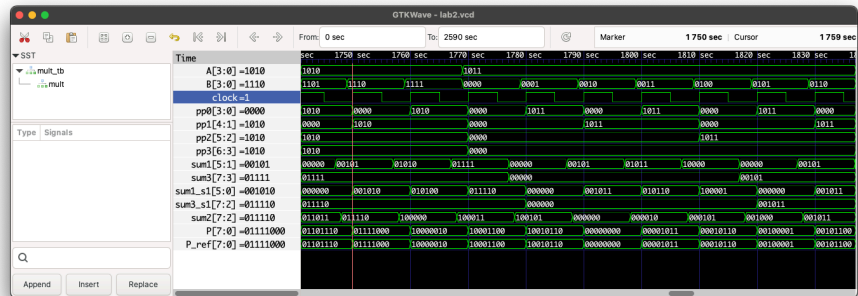

(3)

We can find the latency by the above waveform, for example, if we look at the input at the input at 1750, we have inputs  $A = 1010$  and  $B = 1110$ , which corresponds to 10 and 14 respectively.

Thus, the output  $P$  at 1750 is  $10 \times 14 = 140$ , which can be represented as 10001100 in binary, and this correct product appears at 1770.

Therefore, the latency is  $1770 - 1750 = 20$  ticks.

## 5

### (1)

The minimum clock cycle is 8 ticks

### (2)

The waveform is as follows:

