

# Digital Systems Design and Laboratory

## [ 12. Registers and Counters ]

Chung-Wei Lin

[cwlin@csie.ntu.edu.tw](mailto:cwlin@csie.ntu.edu.tw)

CSIE Department

National Taiwan University

# Sequential Logic Design

## ❑ Unit 11: Latches and Flip-Flops

差別：flip-flop 只有在 active edge 才會改變  
相同：都有記憶功能

➤ Basic unit

## ❑ Unit 12: Registers and Counters

➤ Simple sequential circuit

## ❑ Units 13--15: Finite State Machines

➤ Complex sequential circuit

## ❑ Unit 16: Summary

➤ Put it all together

# Outline

## ☐ **Registers and Register Transfers**

☐ Shift Registers

☐ Design of Binary Counters


☐ Counters for Other Sequences

☐ Counter Design Using S-R and J-K Flip-Flops

☐ Derivation of Flip-Flop Input Equations

# Registers (1/2)

可以想成一對 flip-flop 會接在一起同時運作

 


❑ **Register:** a group of D flip-flops with a common clock

❑ **Example**

➤ 4-bit D flip-flop registers with Data, Load, Clear (ClrN), Clock (Clk)


❑ **First Implementation: gated clock**

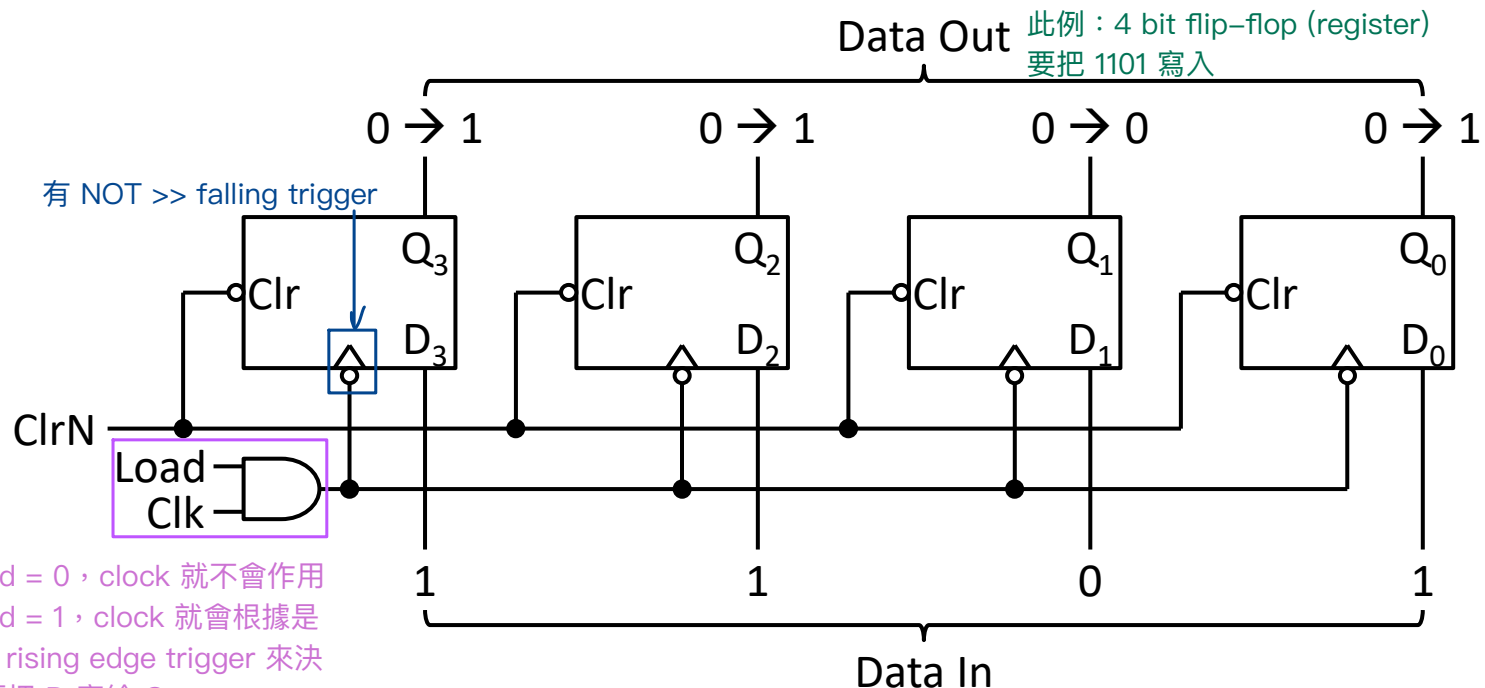➤ When Load = 1, load data at D to Q at Clk falling



- 如果 load = 0，clock 就不會作用
- 如果 load = 1，clock 就會根據是 falling / rising edge trigger 來決定要不要把 D 寫給 Q

# Registers (2/2)

 


❑ Register: a group of D flip-flops with a common clock

❑ Example

➤ 4-bit D flip-flop registers with Data, Load, Clear (ClrN), Clock (Clk)

❑ Second implementation: clock enable

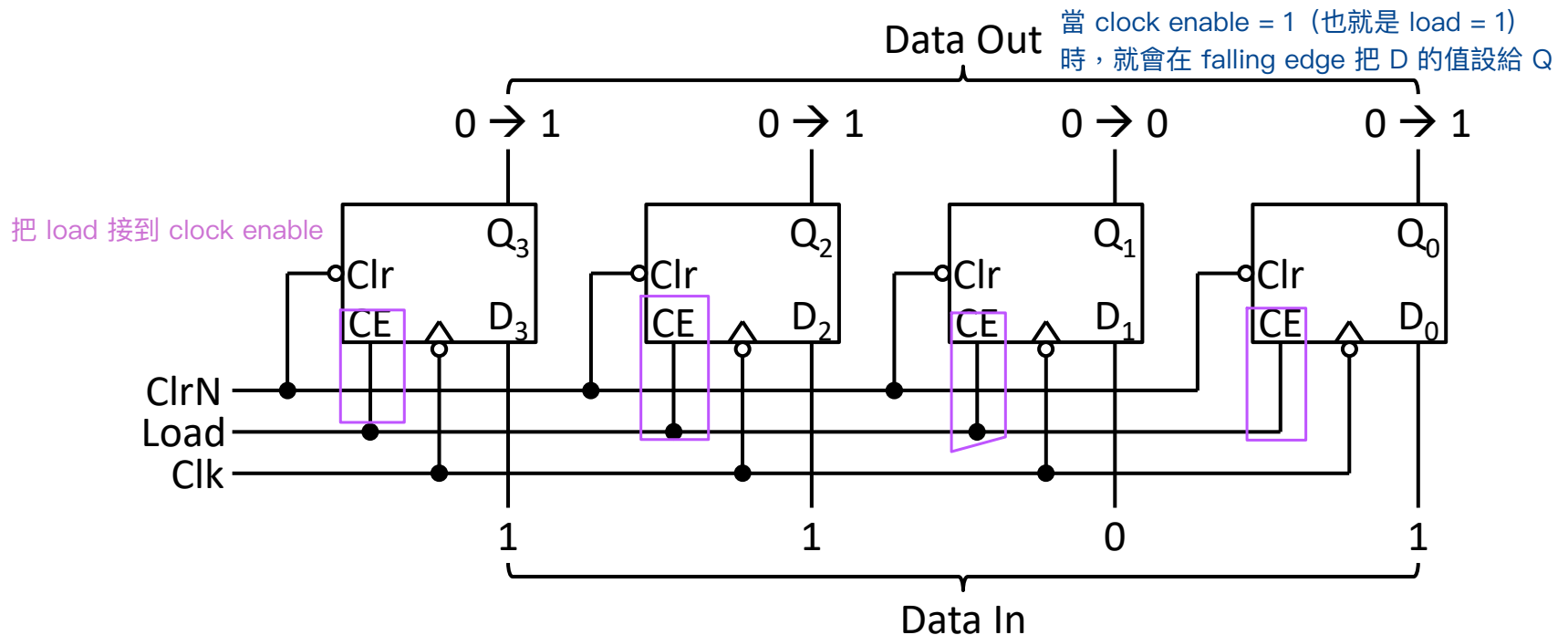➤ When Load = 1, load data at D to Q at Clk falling




# Data Transfer between Registers

## 2-to-1 MUX

- If  $En = 1$ ,  $Q = A$
- If  $En = 0$ ,  $Q = B$   
(enable)


當  $enable = 1$  時，下面兩個  
buffer 被關起來（上面的  
buffer 被打開）

$enable = 0$  則相反

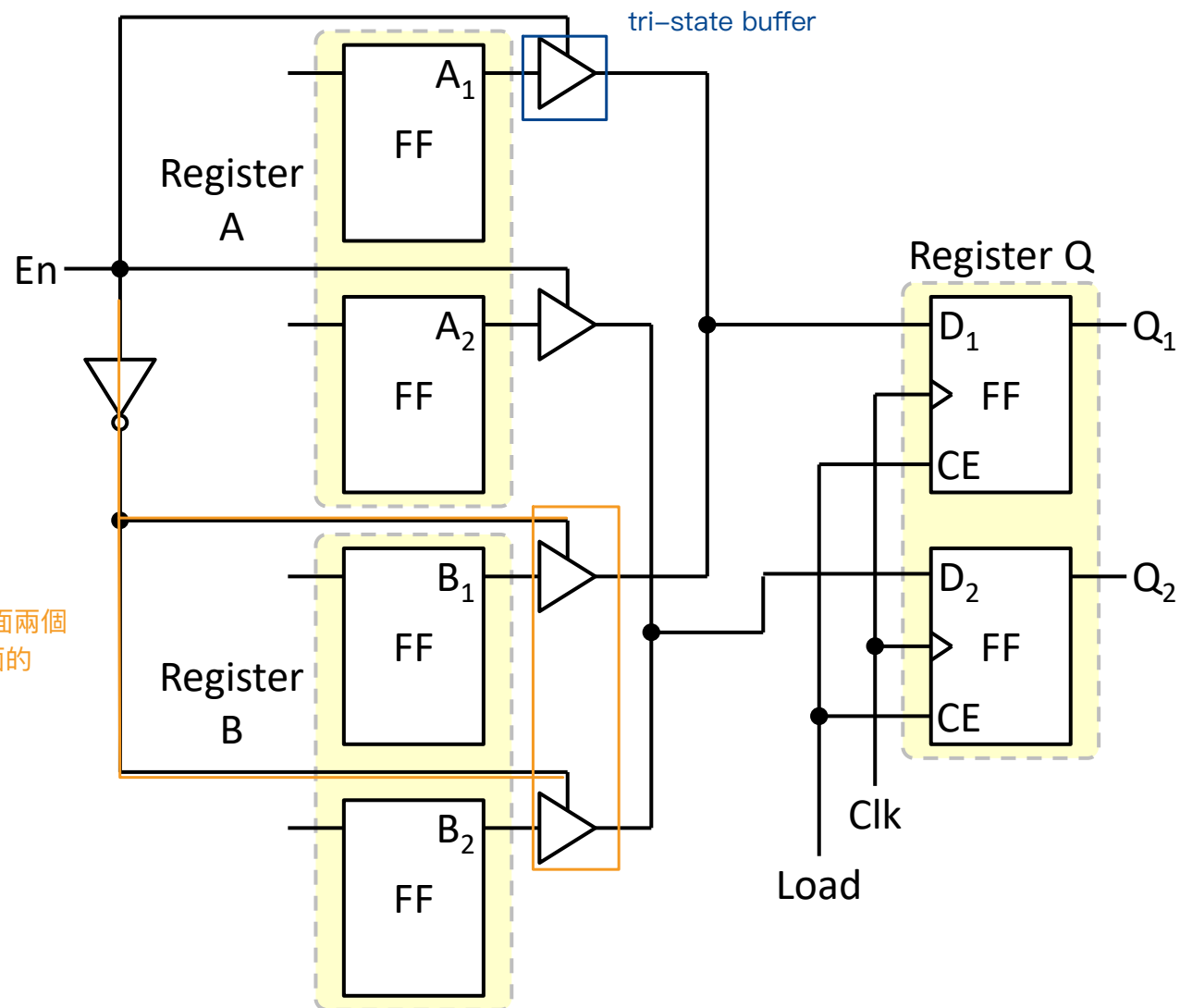


# 8-Bit Register with Tri-State Output (1/2)

## □ Symbol

 


## □ Logic diagram

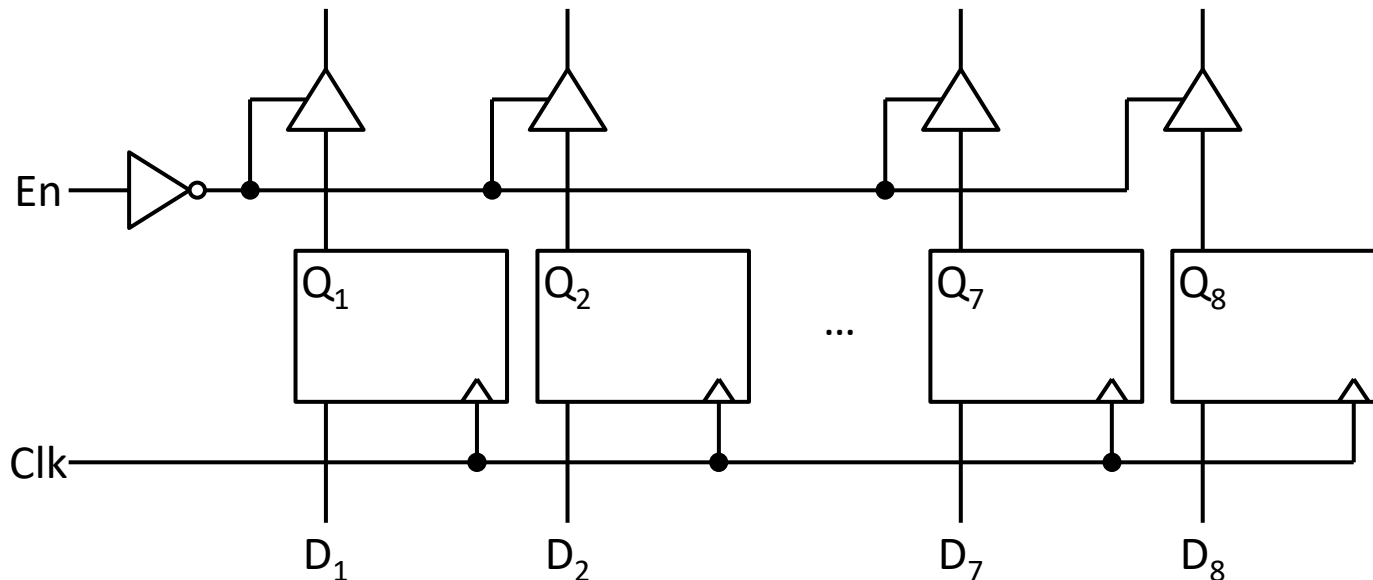

# 8-Bit Register with Tri-State Output (2/2)

## □ Data transfer

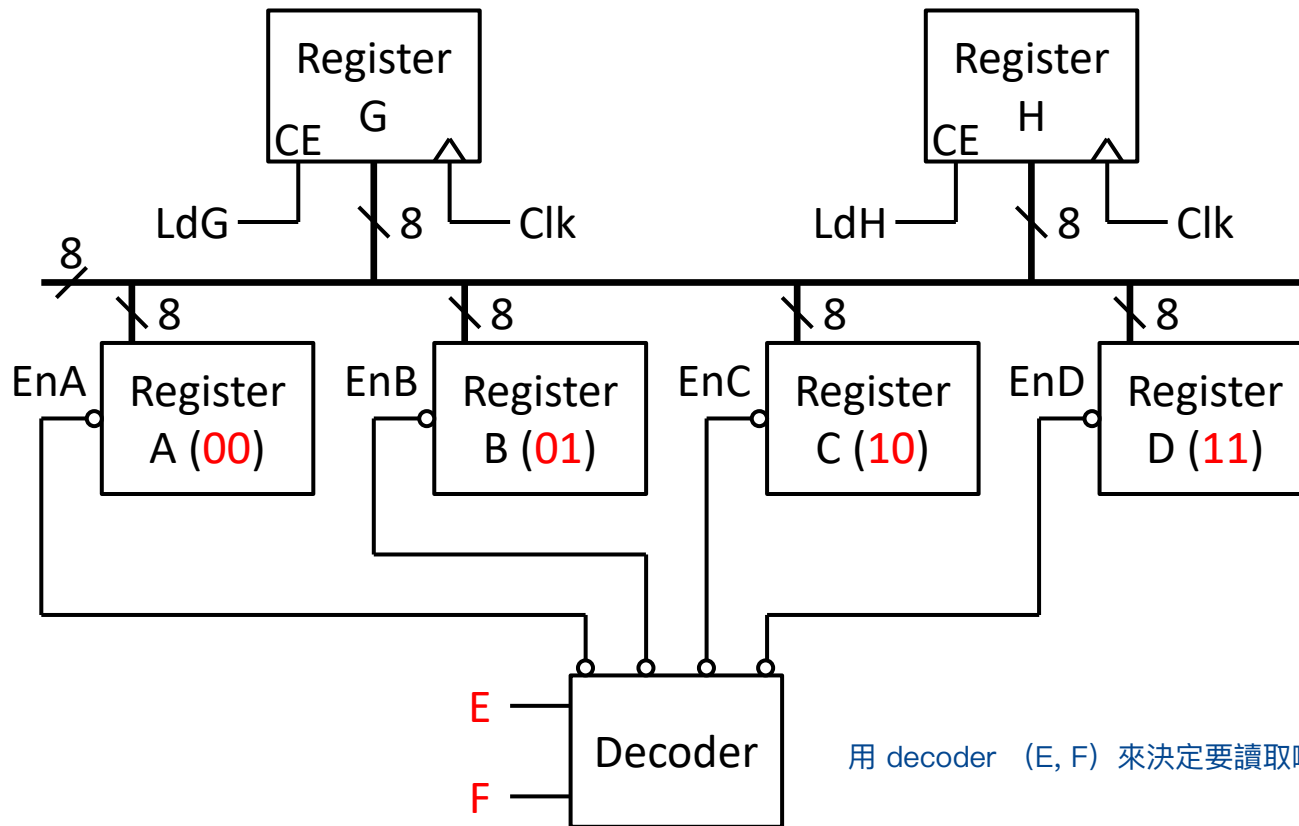

用 decoder (E, F) 來決定要讀取哪個 register 的值

ex: EF = 10

>> register C turn on, 其餘 turn off




# Outline

- ❑ Registers and Register Transfers
- ❑ **Shift Registers**
- ❑ Design of Binary Counters
- ❑ Counters for Other Sequences
- ❑ Counter Design Using S-R and J-K Flip-Flops
- ❑ Derivation of Flip-Flop Input Equations
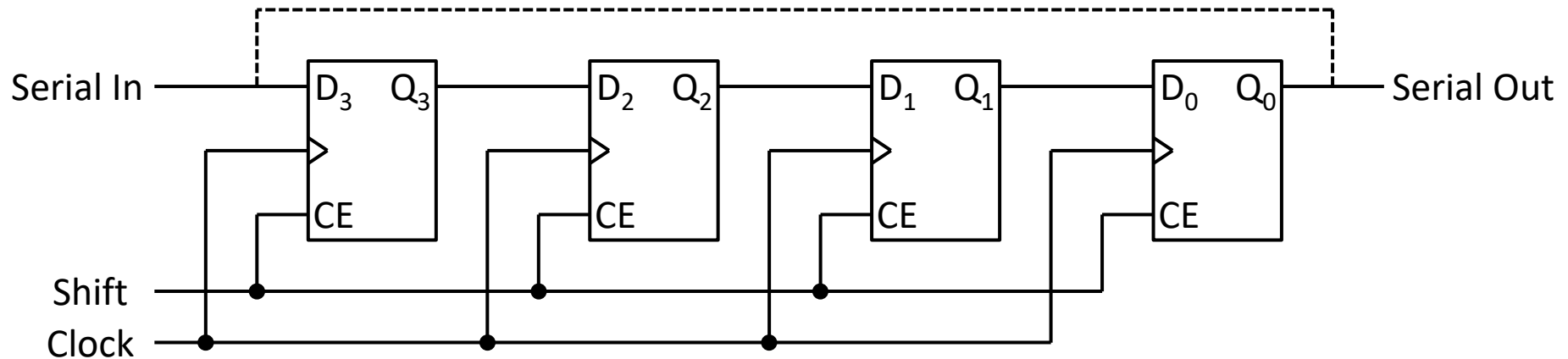
# Shift Registers (1/2)



也是 group of flip-flops，前面的 flip-flop 的 output 會傳給下個 flip-flop

- ❑ Shift register: a group of flip-flops where binary data can be stored and shifted left or right when a shift signal is applied
- ❑ Example: 4-bit right-shift register



# Shift Registers (2/2)
 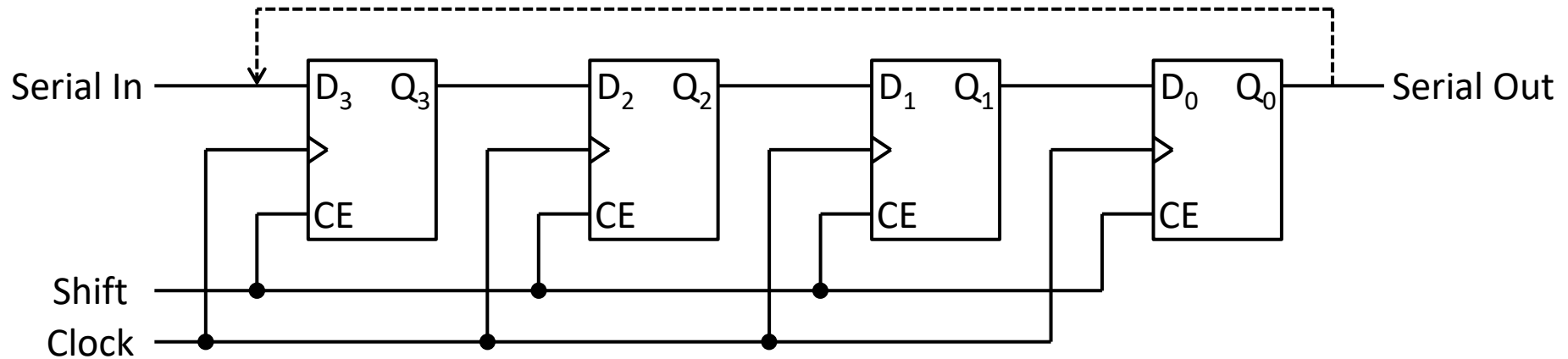
## □ Timing diagram of a 4-bit right-shift register



Initial  $Q_3Q_2Q_1Q_0 = 0101$

SI = 1, 1, 0, 1

$Q_3Q_2Q_1Q_0 =$

在  $t_1$  的 rising edge 時，SI 的 1 寫入  $Q_3$ ， $Q_3$  的值 shift 到  $Q_2$ ， $Q_2$  的值 shift 到  $Q_1$ ，以此類推，最後一個  $Q_0$  的 1 被擠掉


每次 rising edge  $Q_3$  的值就不見了，其餘平移 11

# N-bit Serial-In Serial-Out Shift Registers

❑ Take (n-1) cycles to output data

➤ SI: Serial In

➤ SO: Serial Out

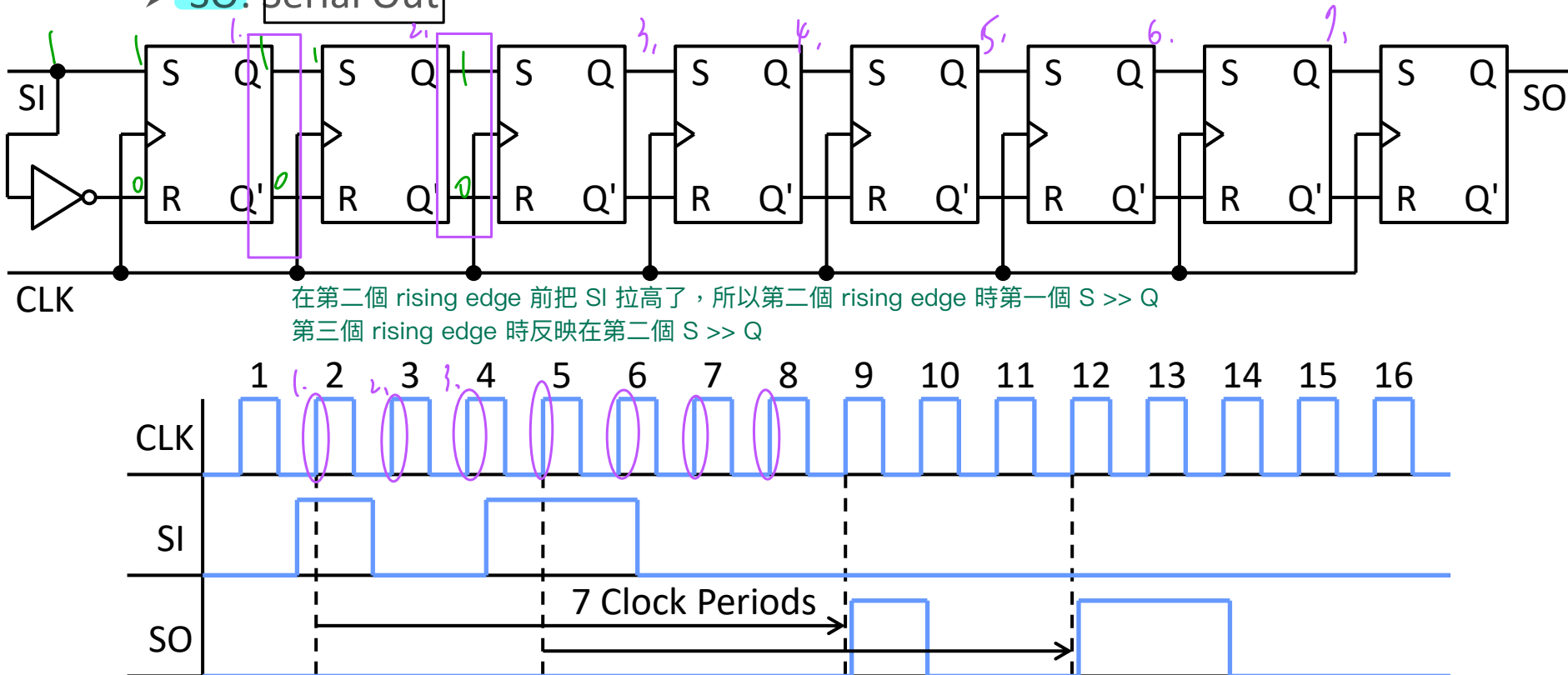

# Parallel-In Parallel-Out Right Shift Register (1/2)

## Parallel-in parallel-out (PIPO)

- Load all data at the same time
- Read out data at the same time


next state equations

$$Q_3^+ = Sh' \cdot L' \cdot Q_3 + Sh' \cdot L \cdot D_3 + Sh \cdot SI$$

$$Q_2^+ = Sh' \cdot L' \cdot Q_2 + Sh' \cdot L \cdot D_2 + Sh \cdot Q_3$$

$$Q_1^+ = Sh' \cdot L' \cdot Q_1 + Sh' \cdot L \cdot D_1 + Sh \cdot Q_2$$
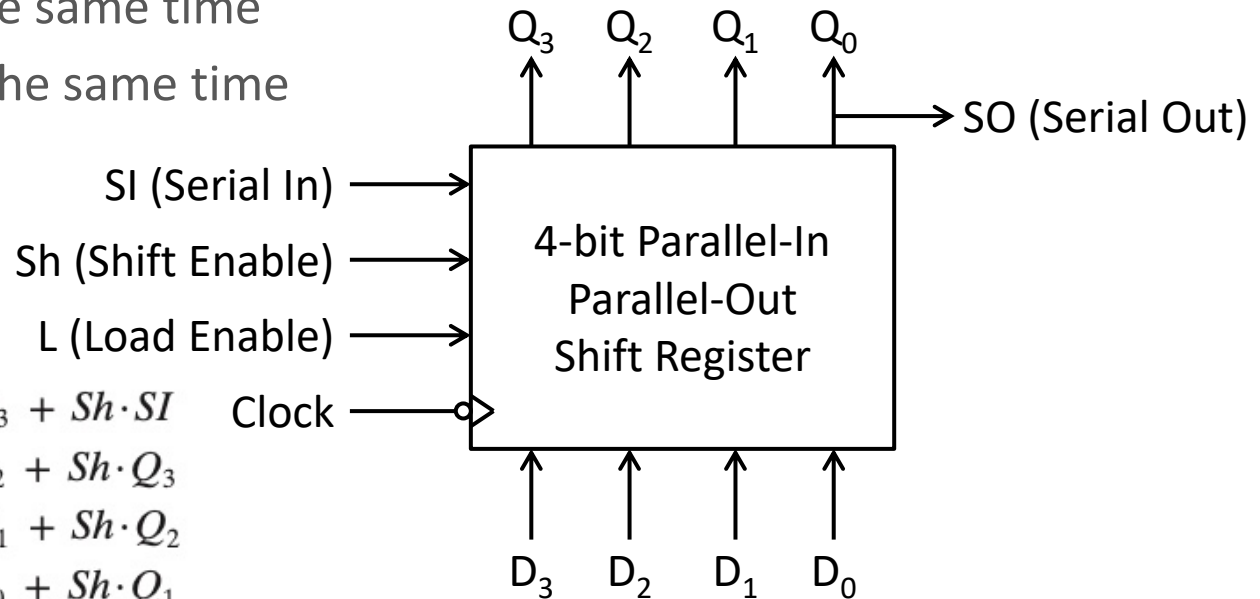
$$Q_0^+ = Sh' \cdot L' \cdot Q_0 + Sh' \cdot L \cdot D_0 + Sh \cdot Q_1$$




Sh (Shift)	L (Load)	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$	Action
0	0	$Q_3$	$Q_2$	$Q_1$	$Q_0$	No Change
0	1	$D_3$	$D_2$	$D_1$	$D_0$	Load
1	X	SI	$Q_3$	$Q_2$	$Q_1$	Right Shift

shift = 1 時，不管 load 是多少都做平移

# Parallel-In Parallel-Out Right Shift Register (2/2)

## Implement using flip-flops and MUXes

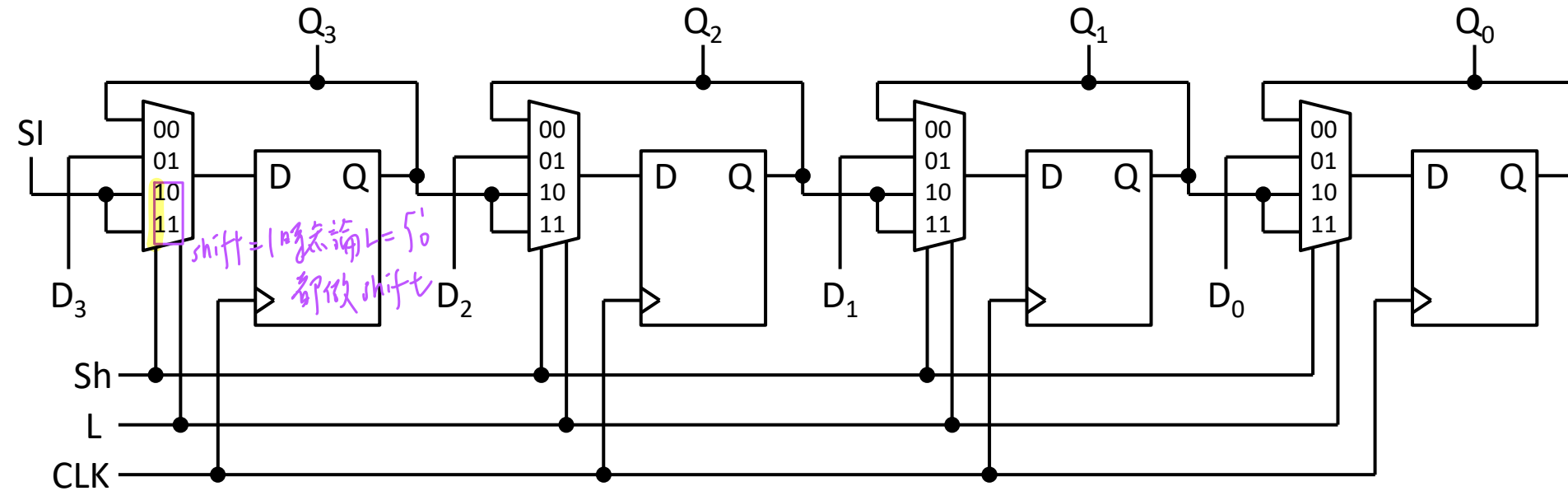


Sh (Shift)	L (Load)	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$	Action
0	0	$Q_3$	$Q_2$	$Q_1$	$Q_0$	No Change
0	1	$D_3$	$D_2$	$D_1$	$D_0$	Load
1	X	SI	$Q_3$	$Q_2$	$Q_1$	Right Shift

 
# Shift Register with Inverted Feedback

❑ Johnson counter: a shift register with inverted feedback

➤ Counter: a circuit that cycles through a fixed sequence of states



❑ State graph

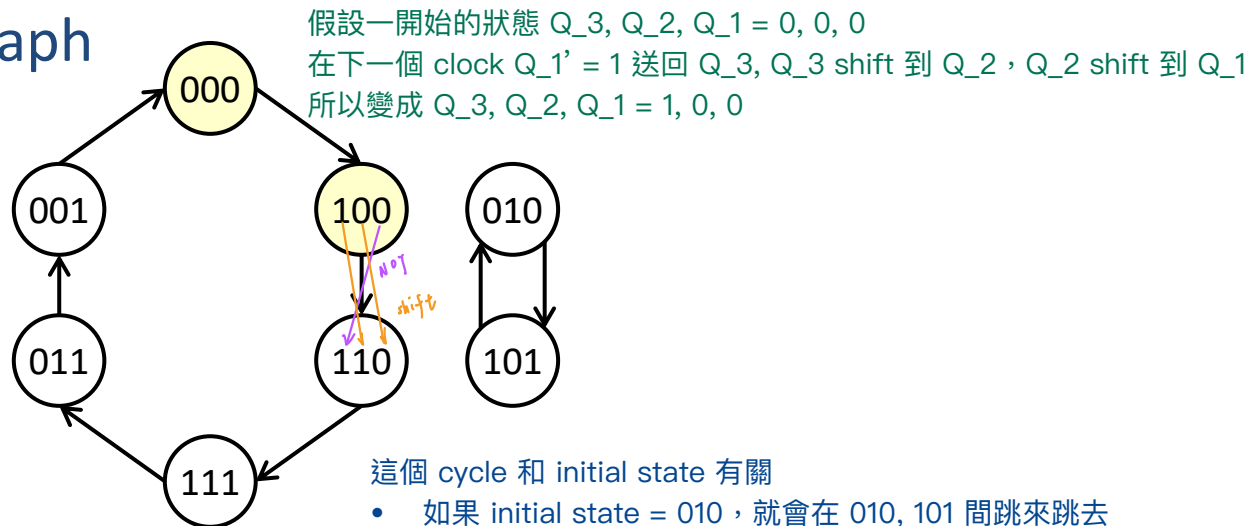

# Outline

- ❑ Registers and Register Transfers
- ❑ Shift Registers
- ❑ **Design of Binary Counters**
- ❑ Counters for Other Sequences
- ❑ Counter Design Using S-R and J-K Flip-Flops
- ❑ Derivation of Flip-Flop Input Equations



T flip-flop : 決定翻轉或不翻轉

D flip-flop : 直接給值

$$Q^+ = D$$

(when edge is triggered)

所有 flip-flop 受同個 clock 控制

❑ **Synchronous counter**: flip-flops are synchronized by a clock

❑ **First implementation: T flip-flops**

$T = 1$  : 翻轉,  $T = 0$  : 不變


Present State			Next State			Flip-Flop Inputs (By Observation)		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

binary counter : 我們想從 0 數到 7 , 到 7 以後再回到 0

# Counting 0--7 (1/2)

用 K-map 做 minimization 來決定 T<sub>B</sub>, T<sub>C</sub>

BA	C	
	0	1
00	0	0
01	0	0
11	1	1
10	0	0

 


因為每次 A 都會改變 (01 交替出現)  
所以 T<sub>A</sub> 固定設為 1 (每次都做翻轉)

# Counting 0--7 (2/2)

D 的值給多少，就會在 active edge 時把 D 的值給多少
 
## Second implementation: D flip-flops

- $D_A = A^+ = A'$
- $D_B = B^+ = BA' + B'A = B \oplus A$ 
  - B changes when A = 1
- $D_C = C^+ = C'BA + CB' + CA' = C \oplus BA$ 
  - C changes when A = B = 1



Present State			Next State		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

A, B 不同時  $B^+ = 1$


$$A \oplus 1 \begin{cases} A=0: 0 \oplus 1 = 1 \\ A=1: 1 \oplus 1 = 0 \end{cases}$$

0 變 1, 1 變 0

# Up-Down Counter
 
## □ U and D control "up" and "down"

- Do not allow  $U = D = 1$
- $D_A = A^+ = A \oplus (U + D)$
- $D_B = B^+ = B \oplus (UA + DA')$  *原:  $B \oplus A$*
- $D_C = C^+ = C \oplus (UBA + DB'A')$  *原:  $C \oplus BA$*




CBA	C <sup>+</sup> B <sup>+</sup> A <sup>+</sup>	
	U	D
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

# Outline

- ❑ Registers and Register Transfers
- ❑ Shift Registers
- ❑ Design of Binary Counters
- ❑ **Counters for Other Sequences**
- ❑ Counter Design Using S-R and J-K Flip-Flops
- ❑ Derivation of Flip-Flop Input Equations
 
# State Diagram of Counter

❑ What if the sequence is not in straight binary order?



Present State			Next State		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

# K-Map Derivation

## Next states

記得注意 midterm 順序

		C	
		0	1
BA	00	1	1
	01	X	X
	11	0	0
	10	0	X

$C^+$

		C	
		0	1
BA	00	0	1
	01	X	X
	11	0	1
	10	1	X

$B^+$

		C	
		0	1
BA	00	0	1
	01	X	X
	11	0	0
	10	1	X

$A^+$

C	B	A	$C^+$	$B^+$	$A^+$
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

# Implementation: T Flip-Flops (1/2)

□ T inputs:  $T = Q \oplus Q^+$

翻 C = 1 時

BA \ C	0	1
00	1	0
01	X	X
11	0	1
10	0	X

$$T_C = C'B' + CB$$

翻 B = 1 時

BA \ C	0	1
00	0	1
01	X	X
11	1	0
10	0	X

$$T_B = C'A + CB'$$

翻 A = 1 時

BA \ C	0	1
00	0	1
01	X	X
11	1	1
10	1	X

$$T_A = C + B$$

(T=1)  
加?


C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

灰底的地方：值改變

白底的地方：值不變

>> T 決定的不是最後的值，而是要不要翻轉

# Implementation: T Flip-Flops (2/2)

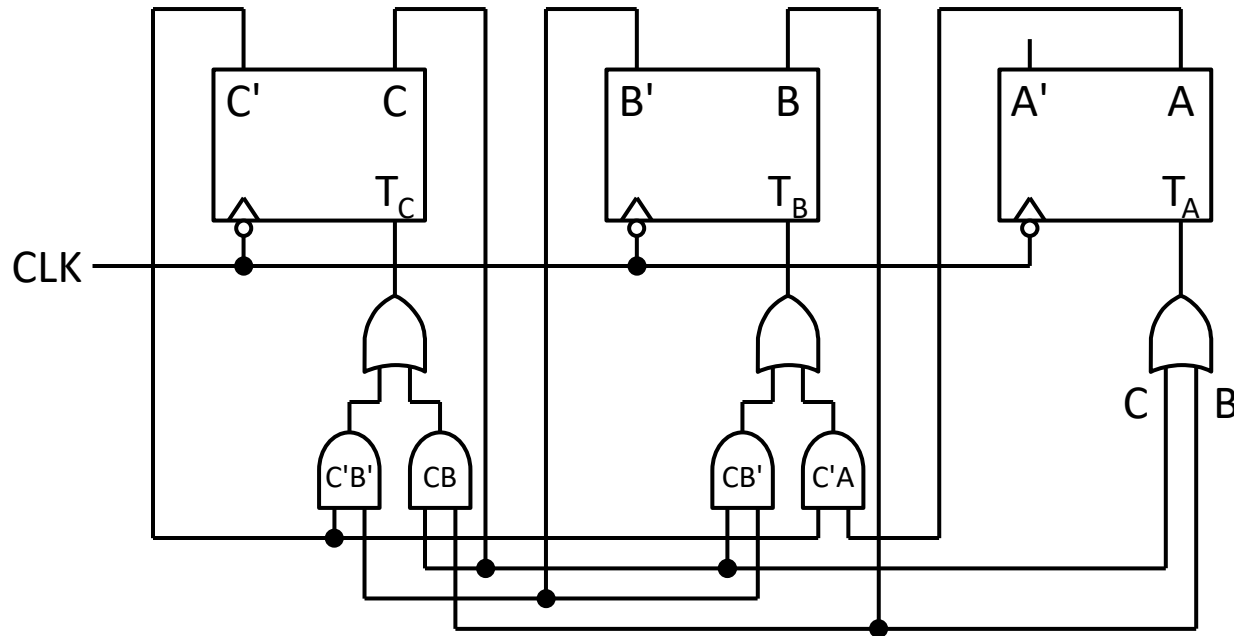




# Don't Care States

如果 initial state 是 don't care
 
## ❑ If flip-flops are initially set to CBA = 001

- Tracking signals through the network shows that  $T_C = T_B = 1$  and  $T_A = 0$ , so the state changes to 111



$$\begin{aligned} T_C &= C'B + CB' = 1 \cdot 1 + 0 \cdot 0 = 1 \rightarrow \text{flip} \\ T_B &= CA + CB' = 1 \cdot 1 + 0 \cdot 1 = 1 \rightarrow \text{flip} \\ T_A &= CB = 0 + 0 = 0 \rightarrow \text{Not flip} \end{aligned}$$

$\therefore CBA = 001 \Rightarrow 111$

## ❑ When the power is turned on, the initial states of all flip-flops are unpredictable!!

在設計時要考慮這些 don't care state 會不會回到 cycle 中

- Don't care states should be checked to make sure that they eventually lead into the main counting sequence
- Or use power-up reset 強迫回到這五個 state 的某個 state

# Implementation: D Flip-Flops (1/2)

next state >> 看 D 送什麼值就是什麼值

## Next states

		C	
		0	1
BA	00	1	1
	01	X	X
11	11	0	0
	10	0	X

$$D_C = B'$$

		C	
		0	1
BA	00	0	1
	01	X	X
11	11	0	1
	10	1	X


$$D_B = C + BA'$$

		C	
		0	1
BA	00	0	1
	01	X	X
11	11	0	0
	10	1	X

$$D_A = CA' + BA'$$

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

# Implementation: D Flip-Flops (2/2)

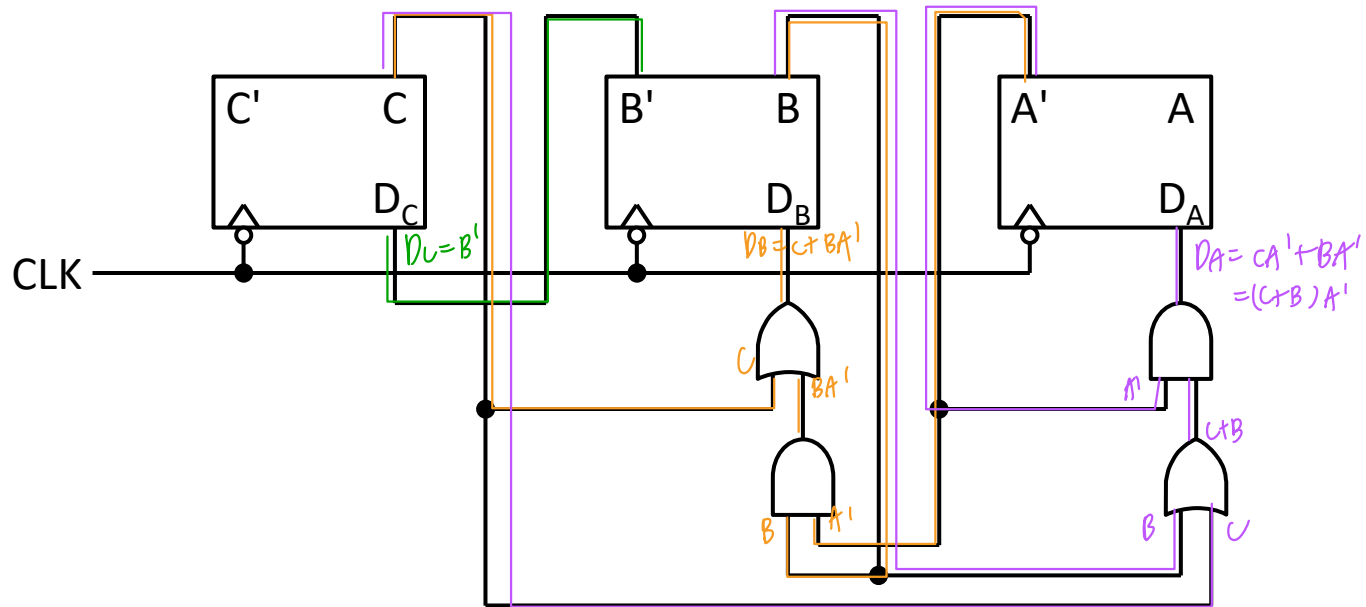

# Outline

- ❑ Registers and Register Transfers
- ❑ Shift Registers
- ❑ Design of Binary Counters
- ❑ Counters for Other Sequences
- ❑ **Counter Design Using S-R and J-K Flip-Flops**
- ❑ Derivation of Flip-Flop Input Equations

# Recap: S-R Flip-Flops

## What is the relation between S, R and Q, Q<sup>+</sup>?

- We do it reversely from Q and Q<sup>+</sup> to S and R
- 因為有兩個 cases 是 not allowed，所以只有六個 cases

S	R	Q	Q <sup>+</sup>		Q	Q <sup>+</sup>	S	R		Q	Q <sup>+</sup>	S	R
0	0	0	0	} $SR=00$ Unchanged	0	0	0	0	} $SR=00$ Unchanged	0	0	0	0
0	0	1	1		0	0	0	1		0	0	0	1
0	1	0	0	} $SR=01$ Reset to 0	0	1	1	0	} $SR=01$ Reset to 0	0	1	1	0
0	1	1	0		1	0	0	1		1	0	0	1
1	0	0	1	} $SR=10$ Set to 1	1	0	0	1	} $SR=10$ Set to 1	1	0	0	1
1	0	1	1		1	1	0	0		1	1	X	0
1	1	0	X	} $SR=11$ Inputs Not Allowed	1	1	0	0	} $SR=11$ Inputs Not Allowed	1	1	X	0
1	1	1	X										


原本的想法：知道 SR，去決定 Q<sup>+</sup>

Excitation Table

這邊變成假如知道 Q >> Q<sup>+</sup>，問 SR = ?

# Using S-R Flip-Flops (1/2)
 
## Derive S-R flip-flop inputs from the excitation table



Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

excitation table



C 從 0 變成 C<sup>+</sup> = 1  
 >> 查 excitation table, QQ<sup>+</sup> = 01, 因此 SR = 10, 所以這邊的 S, C = 1, S, R = 0

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	S <sub>C</sub>	R <sub>C</sub>	S <sub>B</sub>	R <sub>B</sub>	S <sub>A</sub>	R <sub>A</sub>
0	0	0	1	0	0	1	0	0	X	0	X
0	0	1	-	-	-	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	0	0	0	0	X	0	1	0	1
1	0	0	1	1	1	X	0	1	0	1	0
1	0	1	-	-	-	X	X	X	X	X	X
1	1	0	-	-	-	X	X	X	X	X	X
1	1	1	0	1	0	0	1	X	0	0	1

By Karnaugh maps

$$S_C = B', R_C = A, S_B = C, R_B = C'A, S_A = CA' + BA', R_A = A$$

# Using S-R Flip-Flops (2/2)

- truth table 和 K-map 其實是同一件事情

## Alternative: derive S-R flip-flop inputs with K-maps (faster?)

Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

此格代表  $C^+ = 1$ ，也就是： $CC^+ = 01$   
 >> 查 excitation table 發現  $QQ^+ = 01$  對應到 SR = 10

		C	
		0	1
BA	00	1	1
	01	X	X
11	11	0	0
	10	0	X

$C^+$

		C	
		0	1
BA	00	1	X
	01	X	X
11	11	0	0
	10	0	X

$S_C = B'$

		C	
		0	1
BA	00	0	0
	01	X	X
11	11	X	1
	10	X	X

$R_C = A$

# Recap: J-K Flip-Flops

## What is the relation between J, K and Q, Q<sup>+</sup>?

➤ We do it reversely from Q and Q<sup>+</sup> to J and K

如果 Q 要從 0 變成 1，代表 J 必為 1  
(無論是要用 set to 1 還是 toggle 的方式來變，J 都是 1)

J	K	Q	Q <sup>+</sup>	
0	0	0	0	} Unchanged
0	0	1	1	
0	1	0	0	} JK=01 Reset to 0
0	1	1	0	
1	0	0	1	} JK=10 Set to 1
1	0	1	1	
1	1	0	1	} JK=11 Toggle (反轉)
1	1	1	0	

(除 J=1, K=1)  
似 S 似 R  
↓ ↓  
JK=0


Q	Q <sup>+</sup>	J	K	
0	0	0	0	unchanged
0	0	0	1	
0	1	1	0	set
0	1	1	1	
1	0	0	1	reset
1	0	1	1	
1	1	0	0	unchanged
1	1	1	0	

如果 Q, Q<sup>+</sup> 是什麼值，J, K 是什麼值


 
# Using J-K Flip-Flops

- Derive J-K flip-flop inputs from the excitation table



Q	Q <sup>+</sup>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0




C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	J <sub>C</sub>	K <sub>C</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>A</sub>	K <sub>A</sub>
0	0	0	1	0	0	1	X	0	X	0	X
0	0	1	-	-	-	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	0	0	0	0	X	X	1	X	1
1	0	0	1	1	1	X	0	1	X	1	X
1	0	1	-	-	-	X	X	X	X	X	X
1	1	0	-	-	-	X	X	X	X	X	X
1	1	1	0	1	0	X	1	X	0	X	1

By Karnaugh maps


$$J_C = B', K_C = A, J_B = C, K_B = C'A, J_A = C + B, K_A = 1$$

# Implementation

## □ S-R flip-flops

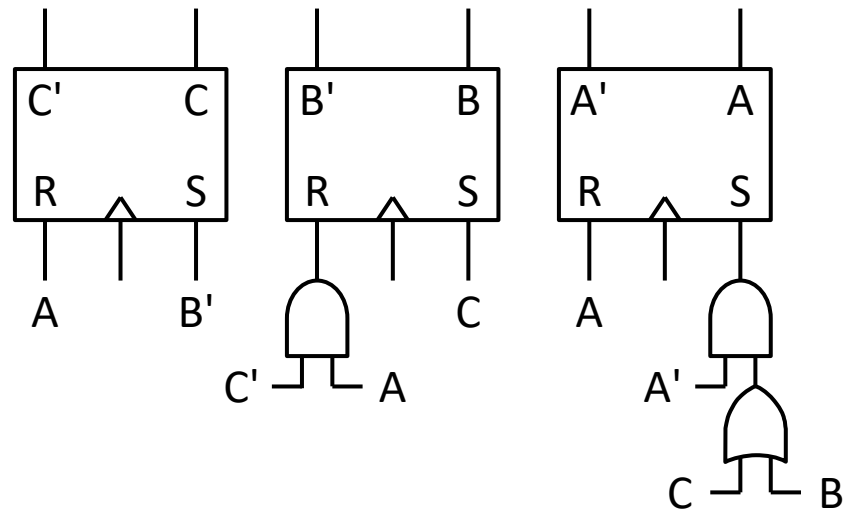

## □ J-K flip-flops

 

# Outline

- ❑ Registers and Register Transfers
- ❑ Shift Registers
- ❑ Design of Binary Counters
- ❑ Counters for Other Sequences
- ❑ Counter Design Using S-R and J-K Flip-Flops
- ❑ **Derivation of Flip-Flop Input Equations**

# Derivation of Flip-Flop Input Equations

- Determine the flip flop input equations from the next-state equations using K-maps

➤ Always copy X's from next state maps onto input maps first

open book 考試記得必定  
要帶這個表!!!

Type of FF	Input	Q = 0		Q = 1		Rules for forming input map from next state map	
		Q <sup>+</sup> = 0	Q <sup>+</sup> = 1	Q <sup>+</sup> = 0	Q <sup>+</sup> = 1	Q = 0 Half of Map	Q = 1 Half of Map
D	D	0	1	0	1	No change	No change
T	T	0	1	1	0	No change	Complement
S-R	S	0	1	0	X	No change	Replace 1's with X's
	R	X	0	1	0	Replace 0's with X's Replace 1's with 0's	Complement
J-K	J	0	1	X	X	No change	Fill in with X's
	K	X	X	1	0	Fill in with X's	Complement

↳ SR, JK 不確定的話可以回去看 excitation table

(excitation table)

# Important Tables

Q	Q <sup>+</sup>	D
0	0	0
0	1	1
1	0	0
1	1	1

D Flip-Flop

Q	Q <sup>+</sup>	T
0	0	0
0	1	1
1	0	1
1	1	0

T Flip-Flop

Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

S-R Flip-Flop

Q	Q <sup>+</sup>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

J-K Flip-Flop

# 3-Variable Example (1/3)

AB \ Q	0	1
00	0	1
01	1	0
11	0	0
10	1	X

$Q^+$



AB \ Q	0	1
00	0	1
01	1	0
11	0	0
10	1	X

$$D = Q'A'B + QB' + AB'$$

p.36 表：

無論是  $Q = 0$  or  $Q = 1$  表都不要變

AB \ Q	0	1
00	0	0
01	1	1
11	0	1
10	1	X

$$T = A'B + AB' + QB$$

p.36 表：

$Q = 0$  半邊不變

$Q = 1$  半邊取 complement (反轉)

# 3-Variable Example (2/3)

AB \ Q		0	1
00		0	1
01		1	0
11		0	0
10		1	X

$Q^+$



AB \ Q		0	1
00		0	X
01		1	0
11		0	0
10		1	X

$S = AB' + Q'A'B$

AB \ Q		0	1
00		X	0
01		0	1
11		X	1
10		0	X

$R = QB$

- 用 SR
- >> 要兩個 K-map (S, R 各一個)
- >> 原本用 D flip-flop 或 T flip-flop 都只要一個)

# 3-Variable Example (3/3)

		Q	
		0	1
AB	00	0	1
	01	1	0
	11	0	0
	10	1	X

$Q^+$



		Q	
		0	1
AB	00	0	X
	01	1	X
	11	0	X
	10	1	X

$$J = A'B + AB'$$

p.36 表 :

Q = 0 半邊不變

Q = 1 半邊都變 don't care

		Q	
		0	1
AB	00	X	0
	01	X	1
	11	X	1
	10	X	X

$$K = B$$

p.36 表 :

Q = 0 半邊都變 don't care

Q = 1 半邊都取 complement



# 4-Variable Example (1/3)

BC \ Q <sub>1</sub> A	00	01	11	10
00	0	1	0	1
01	X	1	1	0
11	1	X	X	1
10	0	0	0	X

Q<sub>1</sub><sup>+</sup>



BC \ Q <sub>1</sub> A		00	01	11	10
		00	01	11	10
Q <sub>2</sub>	00	0	1	1	0
	01	X	1	0	1
	11	1	X	X	0
	10	0	0	1	X

T<sub>1</sub>

灰底處反轉 (don't care 仍為 don't care)

# 4-Variable Ex. (2/3)

p.36 表：  
SR flip-flop 的 R 在  $Q_2 = 0$  時不變

$Q_2 \rightarrow 0$

AB \ CQ <sub>2</sub>	00	01	11	10
00	1	X	1	0
01	0	0	X	1
11	1	0	X	1
10	X	0	0	1

$Q_2^+$

p.36 表：  
SR flip-flop 的 R 在  $Q_2 = 1$  時 1 變 x

AB \ CQ <sub>2</sub>	00	01	11	10
00	1	X	1	0
01	0	0	X	X
11	X	0	X	X
10	X	0	0	1

$S_2$



AB \ CQ <sub>2</sub>	00	01	11	10
00	0	X	0	X
01	1	1	X	0
11	0	1	X	0
10	X	X	X	0

$R_2$

# 4-Variable Ex. (3/3)

$Q_3 = 0$   
 $\Rightarrow J$  no change

(故意換位置將  $Q_3$  擺在  $C$  前面)

$Q_3 \backslash AB$	00	01	11	10
00	0	0	1	X
01	0	1	X	1
11	X	X	0	0
10	1	1	1	0

$Q_3^+$

$Q_3 = 1$   
 $\Rightarrow J$  用 x 填滿

$Q_3 \backslash AB$	00	01	11	10
00	0	0	1	X
01	0	1	X	1
11	X	X	X	X
10	X	X	X	X

$J_3$



$Q_3 \backslash AB$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	X	X	1	1
10	0	0	0	1

$K_3$

# Q&A