

Digital Systems Design and Laboratory

[4. Applications of Boolean Algebra]

Chung-Wei Lin

cwlin@csie.ntu.edu.tw

CSIE Department

National Taiwan University

Outline

☒ Conversion of English Sentences to Boolean Equations

☐ Combinational Logic Design Using a Truth Table

☐ Minterm and Maxterm Expansions

☐ General Minterm and Maxterm Expansions

☐ Incompletely Specified Functions

☐ Examples of Truth Table Construction

☐ Design of Binary Adders and Subtractors

Objectives

❑ Design a combinational logic circuit starting with a word description (specification) of the desired circuit behavior

❑ Steps


- Translate the word description into a switching function
 - Boolean expression or truth table
- Simplify the function
- Realize it using available logic gates

❑ Example

➤ *word description ex;* (Mary watches TV if and only if it is Monday night and she has finished her homework)

- F: Mary watches TV
- A: It is Monday night
- B: Mary has finished her homework

➤ $F = A \bullet B$

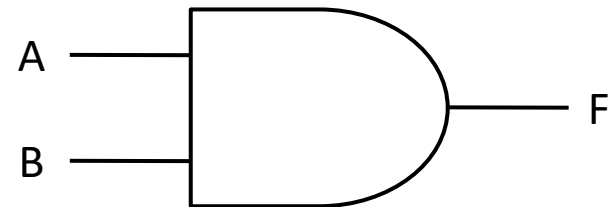


Another Example

❑ The alarm will ring if and only if (the alarm switch is turned on and the door is not closed, or it is after 6pm and the window is not closed)

- Z: The alarm will ring
- A: the alarm switch is on
- B: The door is closed
- C: It is after 6pm
- D: The window is closed

❑ $Z = A \bullet B' + C \bullet D'$

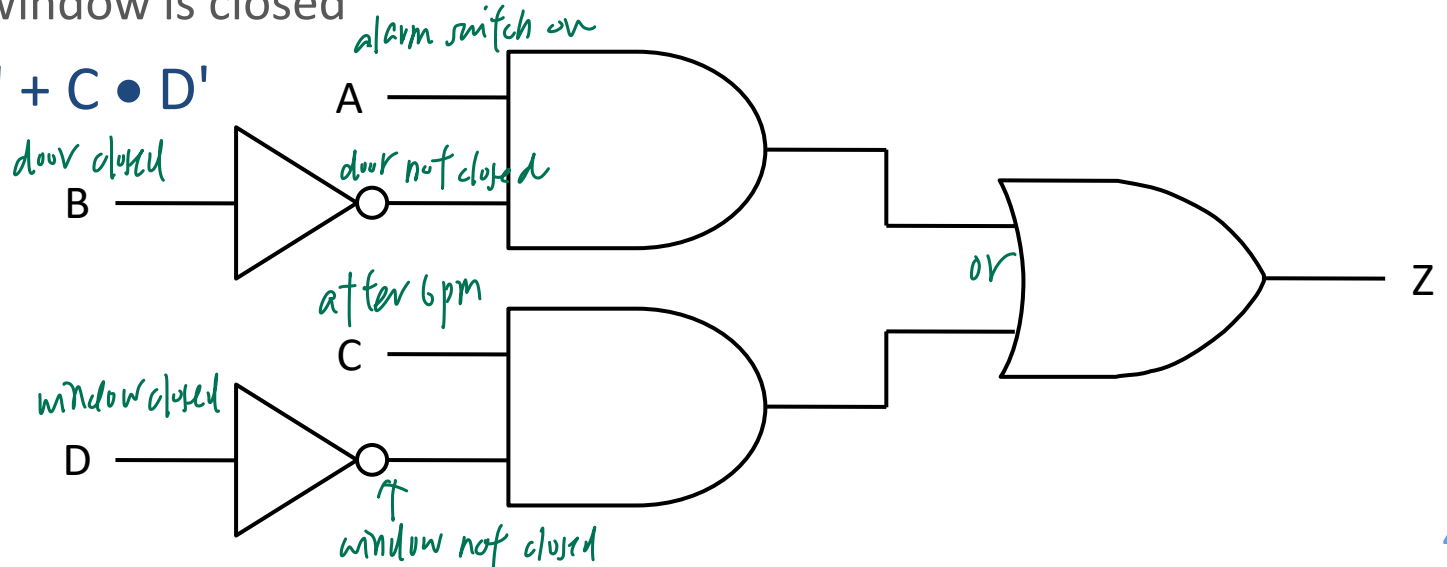

Outline

- ❑ Conversion of English Sentences to Boolean Equations
- ❑ **Combinational Logic Design Using a Truth Table**
- ❑ Minterm and Maxterm Expansions
- ❑ General Minterm and Maxterm Expansions
- ❑ Incompletely Specified Functions
- ❑ Examples of Truth Table Construction
- ❑ Design of Binary Adders and Subtractors


Threshold Detector (1/2)

□ Design a detector that outputs 1 when input is greater than 2

➤ Inputs $(A, B, C)_2$ represent a binary number N

➤ If $N = (A, B, C)_2 \geq 3$, output $F = 1$; otherwise $F = 0$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

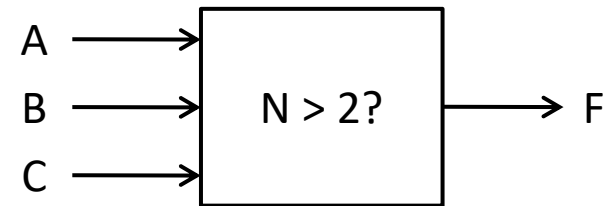


Show the condition to make output = 1

➤ $F = A'BC + AB'C' + AB'C + ABC' + ABC$ (SOP)

$$= \underline{A'BC + ABC} + \underline{AB'C' + AB'C + ABC' + ABC}$$

$$= A + BC$$

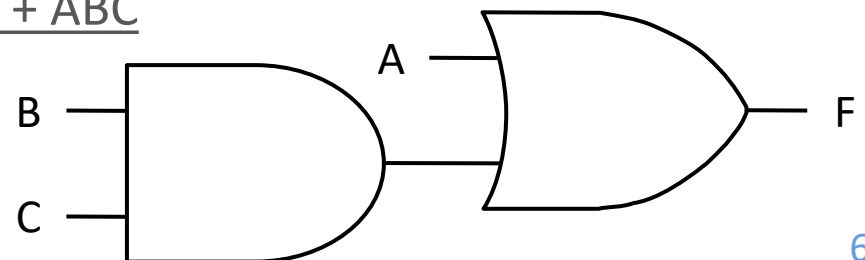↑ ↑
 如果 A=1 如果 A=0
 则所有 唯一可能值 2 即 3
 则 B=1 且 C=1



$$F = A'B + AB'C' + AB'C + ABC' + \textcircled{ABC}$$

$$= \underline{A'BC + ABC} + AB'C' + AB'C + ABC' + ABC$$

$$= (A' + A)BC + AB'(C' + C) + ABC(C' + C)$$

$$= BC + (A'B' + AB)(C' + C)$$

$$= BC + (A'B' + AB)$$

$$= BC + A(B' + B)$$


$$= BC + A$$

Threshold Detector (2/2)

❑ By counting 1's, we have SOP

❑ What if counting 0's

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

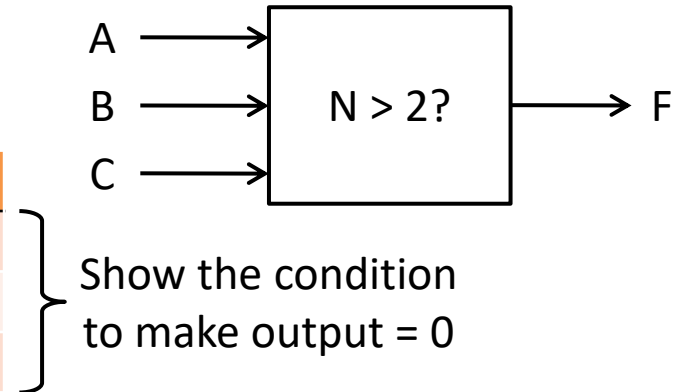

$$\begin{aligned} \text{➤ } F &= (ABC \neq 000) \bullet (ABC \neq 001) \bullet (ABC \neq 010) \\ &= (\overset{0}{A}'\overset{0}{B}'\overset{0}{C}')' \bullet (\overset{0}{A}'\overset{0}{B}'\overset{1}{C})' \bullet (\overset{0}{A}'\overset{1}{B}\overset{0}{C}')' = (A + B + C) \bullet (A + B + C') \bullet (A + B' + C) \end{aligned}$$

$$\begin{aligned} \text{➤ } F &= F'' = (A'B'C' + A'B'C + A'BC')' \leftarrow \text{0,1,2 的情况 0 起来, 取 ' } \\ &= (A'B'C')' \bullet (A'B'C)' \bullet (A'BC')' = (A + B + C) \bullet (A + B + C') \bullet (A + B' + C) \end{aligned}$$


$$\begin{aligned}
 F &= \overset{0 \ 0 \ 0}{(A'B'C')'} \cdot \overset{0 \ 0 \ 1}{(A'B'C)'} \cdot \overset{0 \ 1 \ 0}{(A'BC')} \\
 &= \underline{(A+B+C)} \cdot (A+B+C') \cdot (A+B'+C) \quad \leftarrow \text{POS} \\
 &\quad \text{(product of sums)}
 \end{aligned}$$

$$(X_1 X_2 \dots X_n)' = (X_1' + X_2' + \dots + X_n')$$

Logic Design Using a Truth Table

□ Steps

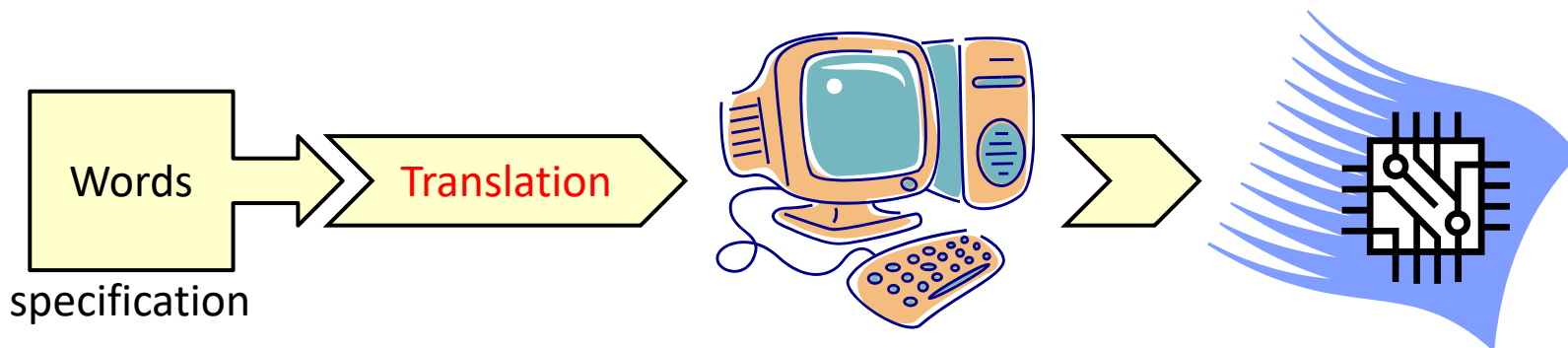- Make a truth table according to the word description
- Generate a Boolean expression
 - Sum-of-products (SOP): check 1's 检查 output = 1 的情况
 - Product-of-sums (POS): check 0's " " = 0 "
 - Have F' in SOP and then derive F in POS
- Simplify the Boolean expression



Outline

- ❑ Conversion of English Sentences to Boolean Equations
- ❑ Combinational Logic Design Using a Truth Table
- ❑ **Minterm and Maxterm Expansions**
- ❑ General Minterm and Maxterm Expansions
- ❑ Incompletely Specified Functions
- ❑ Examples of Truth Table Construction
- ❑ Design of Binary Adders and Subtractors

n variables 要有 n literals, 且每个 variable 同时出现一次

Minterm and Maxterm

Definition: A ^{product}minterm/^{sum}maxterm of n variables is a product/sum of n literals in which each variable appears exactly once in either true or complement form (but not both)

➤ A literal is a variable or its complement (A or A')

➤ Examples of 3 variables

• Minterm: A'BC, AB'C' *A 到 A' 一定要同时出现一个*

• Maxterm: A + B + C, A + B + C'

m_i 和 M_i 是 NOT 的关系
 $(m_i)' = M_i$

Row No.	ABC	Minterm m_i	↔	Maxterm M_i
0	000	$m_0 = A'B'C'$		$M_0 = A + B + C$
1	001	$m_1 = A'B'C$		$M_1 = A + B + C'$
2	010	$m_2 = A'BC'$		$M_2 = A + B' + C$
3	011	$m_3 = A'BC$		$M_3 = A + B' + C'$
4	100	$m_4 = AB'C'$		$M_4 = A' + B + C$
5	101	$m_5 = AB'C$		$M_5 = A' + B + C'$
6	110	$m_6 = ABC'$		$M_6 = A' + B' + C$
7	111	$m_7 = ABC$		$M_7 = A' + B' + C'$

*3 variables
 ⇒ 所有可能:*

*3 = 8 minterms
 2 = 8 maxterms*


Minterm Expansion

□ A minterm expansion or a standard sum of products is a function written as a sum of minterms

➤ Counting 1's *minterm expansion (考虑 n 个 variables 的情况下)*
每个 product 都有 n 个 variables

□ Example

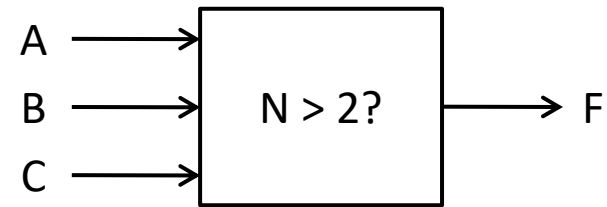➤ $F = A'BC + AB'C' + AB'C + ABC' + ABC$
 $= m_3 + m_4 + m_5 + m_6 + m_7$ (m-notation)
 $= \sum m(3, 4, 5, 6, 7)$ 列表法.



m \Rightarrow minterm

Row No.	ABC	Minterm m_i	Maxterm M_i
0	000	$m_0 = A'B'C'$	$M_0 = A + B + C$
1	001	$m_1 = A'B'C$	$M_1 = A + B + C'$
2	010	$m_2 = A'BC'$	$M_2 = A + B' + C$
3	011	$m_3 = A'BC$	$M_3 = A + B' + C'$
4	100	$m_4 = AB'C'$	$M_4 = A' + B + C$
5	101	$m_5 = AB'C$	$M_5 = A' + B + C'$
6	110	$m_6 = ABC'$	$M_6 = A' + B' + C$
7	111	$m_7 = ABC$	$M_7 = A' + B' + C'$


Maxterm Expansion

- A maxterm expansion or a standard product of sums is a function written as a product of maxterms

➤ Counting 0's *每個 variable 都出現一次*

□ Example

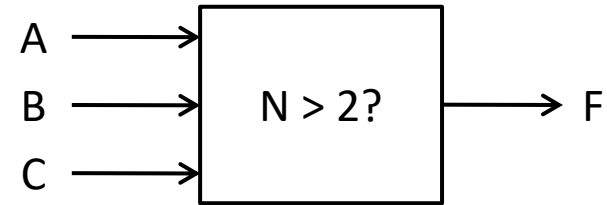➤ $F = (A + B + C) \cdot (A + B + C') \cdot (A + B' + C)$
 $= M_0 M_1 M_2$ (M-notation)
 $= \prod M(0, 1, 2)$



Row No.	ABC	Minterm m_i	Maxterm M_i
0	000	$m_0 = A'B'C'$	$M_0 = A + B + C$
1	001	$m_1 = A'B'C$	$M_1 = A + B + C'$
2	010	$m_2 = A'BC'$	$M_2 = A + B' + C$
3	011	$m_3 = A'BC$	$M_3 = A + B' + C'$
4	100	$m_4 = AB'C'$	$M_4 = A' + B + C$
5	101	$m_5 = AB'C$	$M_5 = A' + B + C'$
6	110	$m_6 = ABC'$	$M_6 = A' + B' + C$
7	111	$m_7 = ABC$	$M_7 = A' + B' + C'$

*總的
情況*



前面例子：

≤ 2 時 output = 0

Complement by Minterms/Maxterms

□ $(m_i)' = M_i$

□ Complement of F

➤ Counting 0's in F (find F' directly)

• $F' = m_0 + m_1 + m_2 = \sum m(0, 1, 2)$

• $F' = M_3 M_4 M_5 M_6 M_7 = \prod M(3, 4, 5, 6, 7)$

$F = \sum m(3, 4, 5, 6, 7)$

$= m_3 + m_4 + m_5 + m_6 + m_7$

$F = \prod M(0, 1, 2)$
 $= M_0 M_1 M_2$

➤ Counting 1's in F (find F and then complement it)

• $F' = (m_3 + m_4 + m_5 + m_6 + m_7)'$
 $= m_3' m_4' m_5' m_6' m_7'$ *de Morgan*
 $= M_3 M_4 M_5 M_6 M_7$
 $= \prod M(3, 4, 5, 6, 7)$

• $F' = (M_0 M_1 M_2)'$
 $= M_0' + M_1' + M_2'$
 $= m_0 + m_1 + m_2$
 $= \sum m(0, 1, 2)$

A	B	C	F	F'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Another Example

□ Example: $F(A, B, C, D) = A'(B' + D) + ACD'$ → 找 minterm expansion
 \Rightarrow sum of products (乘积)

$$F(A, B, C, D)$$

$$= A'(B' + D) + ACD'$$

$$= A'B' + A'D + ACD'$$

$$= A'B'(C + C')(D + D') + A'D(B + B')(C + C') + ACD'(B + B')$$

$$= A'B'C'D' + A'B'C'D + A'B'CD' + A'B'CD + A'BC'D + A'BCD + ABCD' + AB'CD'$$

$$= \sum m(\overset{0}{0000}, \overset{1}{0001}, \overset{2}{0010}, \overset{3}{0011}, \overset{5}{0101}, \overset{7}{0111}, \overset{14}{1110}, \overset{10}{1010}) \quad \dots \text{Minterm Expansion}$$

$$F(A, B, C, D) = A'(B' + D) + ACD' \quad (X + Y)(X + Z) = X + YZ \text{ (distributive)}$$

$$= (A' + CD')(A + B' + D) = (A' + C)(A' + D')(A + B' + D)$$

$$= (A' + BB' + C + DD')(A' + BB' + CC' + D')(A + B' + CC' + D)$$

$$= \dots \quad \dots \quad \dots$$

$$= \prod M(4, 6, 8, 9, 11, 12, 13, 15) \quad \dots \text{Maxterm Expansion}$$

$$(A' + BB' + C + DD') = (A' + B + C + DD') (A' + B' + C + DD')$$

$$\downarrow \downarrow \quad (X + YZ) = (X + Y)(X + Z)$$

$$= [(A'+B+C+D)(A'+B+C+D')][(A'+B'+C+D)(A'+B'+C+D')]$$

Summary

↑
maxterm (product of sums)

❑ Convert a Boolean expression to a minterm/maxterm expansion

➤ Use truth table

min term \Rightarrow 看 1 的 状态 \Rightarrow OR 起来
 max term \Rightarrow 看 0 的 状态 \Rightarrow AND 起来

- Sometimes there are too many terms

❑ Use Boolean algebra

- SOP: multiply out and use $(X + X') = 1 \rightarrow$ minterm expansion (SOP)
- POS: factor and use $XX' = 0 \rightarrow$ maxterm expansion (POS)

↑
缺项 \Rightarrow 补 redundant

Outline

- ❑ Conversion of English Sentences to Boolean Equations
- ❑ Combinational Logic Design Using a Truth Table
- ❑ Minterm and Maxterm Expansions
- ❑ **General Minterm and Maxterm Expansions**
- ❑ Incompletely Specified Functions
- ❑ Examples of Truth Table Construction
- ❑ Design of Binary Adders and Subtractors

General Truth Table

□ Given n Boolean variables, how many different Boolean functions can you produce?

➤ Each a_i can be assigned with either 0 or 1

Boolean function $f \rightarrow 2^{(2^n)}$ 每个 case 都有 1 个 %

n 个 variables

$\Rightarrow 2^n$ 个 cases

A	B	C	F
0	0	0	a_0
0	0	1	a_1
0	1	0	a_2
0	1	1	a_3
1	0	0	a_4
1	0	1	a_5
1	1	0	a_6
1	1	1	a_7

每个 a_i $i=0 \sim 7$ 都可以有 0/1 两值

AND of Minterm Expansions

□ Given $F_1 = \sum m(0, 2, 3, 5, 9, 11)$ and $F_2 = \sum m(0, 3, 9, 11, 13, 14)$,

find $F_1 F_2 = ?$ 这个AND 两边都要是1

➤ AND: take the numbers that appear in both expansions

➤ $F_1 F_2 = \sum m(0, 3, 9, 11)$

□ AND for two maxterm expansions? 留只存在于一边出现的数字.

□ OR for two minterm expansions? 只要出现一次就留下来

□ OR for two maxterm expansions? 都出现才留下来.

$$F_1 = m_0 + m_2 + m_3 + m_5 + m_9 + m_{11}$$

$$F_2 = m_0 + m_3 + m_9 + m_{11} + m_{13} + m_{14}$$

$$\begin{aligned} F_1 \cdot F_2 &= (m_0 + m_2 + m_3 + m_5 + m_9 + m_{11}) (m_0 + m_3 + m_9 + m_{11} + m_{13} + m_{14}) \\ &= m_0 + m_3 + m_9 + m_{11} + (m_2 + m_5)(m_{13} + m_{14}) \end{aligned}$$

Conversion of Forms

❑ Convert between a minterm and a maxterm expansion

Given Form	Desired Form	Minterm Expansion of F	Maxterm Expansion of F	Minterm Expansion of F'	Maxterm Expansion of F'
Minterm Expansion of F		---	The nos. not on the minterm list for F	The minterms not present in F	The same as minterm nos. of F
Maxterm Expansion of F		The nos. not on the maxterm list for F	---	The same as maxterm nos. of F	The maxterms not present in F

Given Form	Desired Form	Minterm Expansion of F	Maxterm Expansion of F	Minterm Expansion of F'	Maxterm Expansion of F'
$F = \sum m(3, 4, 5, 6, 7)$		---	$\prod M(0, 1, 2)$	$\sum m(0, 1, 2)$	$\prod M(3, 4, 5, 6, 7)$
$F = \prod M(0, 1, 2)$		$\sum m(3, 4, 5, 6, 7)$	---	$\sum m(0, 1, 2)$	$\prod M(3, 4, 5, 6, 7)$

max 转 min \rightarrow 翻一次
 F 转 F' \rightarrow 翻一次 \Rightarrow 翻两次 = 原数字


Outline

- ❑ Conversion of English Sentences to Boolean Equations
- ❑ Combinational Logic Design Using a Truth Table
- ❑ Minterm and Maxterm Expansions
- ❑ General Minterm and Maxterm Expansions
- ❑ **Incompletely Specified Functions**
- ❑ Examples of Truth Table Construction
- ❑ Design of Binary Adders and Subtractors

Incompletely Specified Functions (1/2)

- ❑ A large digital system is usually divided into subcircuits
- ❑ Assume N_1 never generates $ABC = 001/110$ for any W, X, Y, Z

A	B	C	F
0	0	0	1
0	0	1	X
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

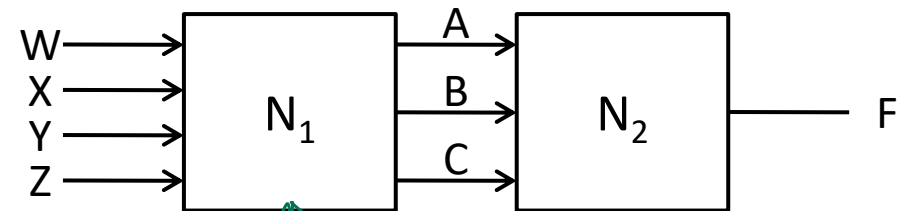

↑
假設 N_1 output
不會產生 001/110

∵ 001/110
不會出現

∵ 001/110 為 input N_1 的 output $\rightarrow X$
(don't care)

- ❑ F: Incompletely specified function

- ❑ $A'B'C, ABC'$: don't care terms

➤ "don't care" (DC) terms can be assigned with either 0 or 1

↓
可為 0 也可為 1

Incompletely Specified Functions (2/2)

□ Impact of don't care terms on Boolean simplification

- Try exhaustive combinations of DCs to find the best
 - (may be stupid but works for now) *1001/110 48 output 0/1 27*
- Assign 0 to both "X" *⇒ 訂正する必要がある*
 - $F = A'B'C' + A'BC + ABC = A'B'C' + BC$
- Assign 1 to 1st "X" and 0 to 2nd "X" (seems to be the simplest)
 - $F = A'B'C' + \underline{A'B'C} + A'BC + ABC = A'B' + BC$
- Assign 1 to both "X"
 - $F = A'B'C' + \underline{A'B'C} + A'BC + \underline{ABC'} + ABC = A'B' + BC + AB$
- ...
- 2. is the simplest solution

A	B	C	F
0	0	0	1
0	0	1	X
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

□ Notation

- $F = \sum m(0, 3, 7) + \sum d(1, 6)$ *min term ⇒ OR*
- $F = \prod M(2, 4, 5) \bullet \prod D(1, 6)$ *max term ⇒ AND*

Outline

- ❑ Conversion of English Sentences to Boolean Equations
- ❑ Combinational Logic Design Using a Truth Table
- ❑ Minterm and Maxterm Expansions
- ❑ General Minterm and Maxterm Expansions
- ❑ Incompletely Specified Functions
- ❑ **Examples of Truth Table Construction**
- ❑ Design of Binary Adders and Subtractors

Error Detector for 6-3-1-1 Codes (1/2)

invalid by output $F=1$

□ Design an error detector for 6-3-1-1 codes:

- The output $F = 1$ iff inputs (A, B, C, D) represent an **invalid** code combination
- Step 1: construct the truth table

Decimal Digit	6-3-1-1 Code
0	0000
1	0001
2	0011
3	0100
4	0101
5	0111
6	1000
7	1001
8	1011
9	1100

	ABCD	F	
0	0000 m_0	0	
1	0001 m_1	0	
2	0010 m_2	1	$A'B'CD'$
3	0011 m_3	0	
4	0101 m_5	0	
5	0110 m_6	1	$A'BCD'$
6	1000 m_7	0	
7	1001 m_8	0	
8	1010 m_9	1	$AB'CD'$
9	1011 m_{10}	0	
10	1101 m_{11}	1	$ABC'D$
11	1110 m_{12}	1	$ABCD'$
12	1111 m_{13}	1	$ABCD$

m_2 or m_6 or m_{10} or m_{11} or m_{14} or m_{15} are invalid

$$\therefore F = m_2 + m_6 + m_{10} + m_{11} + m_{14} + m_{15}$$

$$= \sum m(2, 6, 10, 11, 14, 15)$$

$$= \underline{A'B'CD'} + \underline{A'BCD'} + \underline{AB'CD'} + \underline{ABC'D} + \underline{ABCD'} + \underline{ABCD} \Rightarrow \text{simplify}$$

$$= A'CD'(B'+B) + ACD'(B'+B) + ABD(C+C')$$

$$= \underline{A'CD'} + \underline{ACD'} + ABD$$

$XY + XY' = X$ (uniting)

$$= \underline{CD'} + ABD$$

Error Detector for 6-3-1-1 Codes (2/2)


□ Design an error detector for 6-3-1-1 codes:

➤ The output $F = 1$ iff inputs (A, B, C, D) represent an **invalid** code combination

➤ Step 2: simplify the function

$$\begin{aligned} &F(A, B, C, D) \\ &= \sum m(2, 6, 10, 13, 14, 15) \\ &= \underline{A'B'CD'} + \underline{A'BCD'} + \underline{AB'CD'} + \underline{ABCD'} + \underline{ABC'D} + \underline{ABCD} \\ &= \underline{A'CD'} + \underline{ACD'} + \underline{ABD} \\ &= CD' + ABD \end{aligned}$$

➤ Step 3: realize it

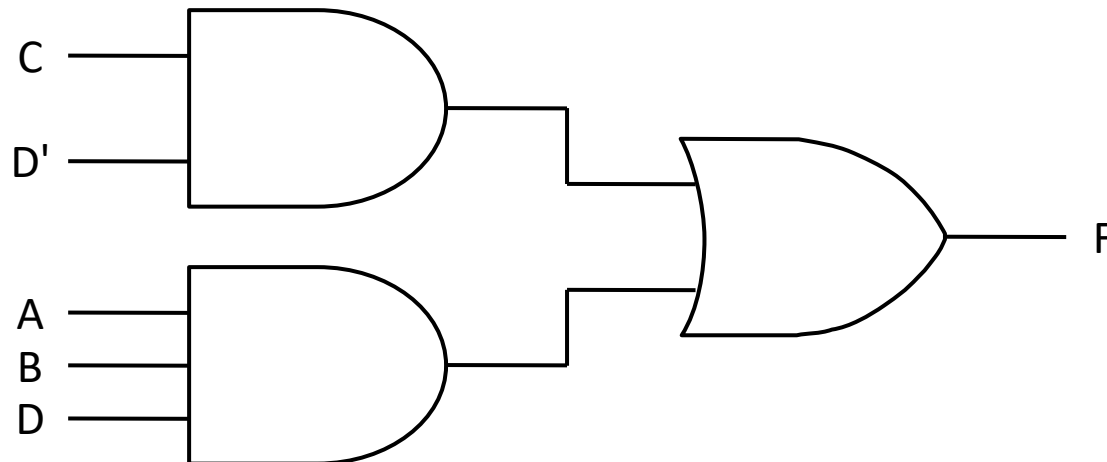

ABCD	F
0000	0
0001	0
0010	1
0011	0
0100	0
0101	0
0110	1
0111	0
1000	0
1001	0
1010	1
1011	0
1100	0
1101	1
1110	1
1111	1

Another Example

□ The output $Z = 1$ iff the 8-4-2-1 BCD number (A, B, C, D) is divisible by 3


➤ Step 1: construct the truth table

➤ Step 2: simplify the function

$$Z(A, B, C, D) = \sum m(0, 3, 6, 9) + \sum d(10, 11, 12, 13, 14, 15)$$

➤ Step 3: realize it

- ?
- Unit 5!

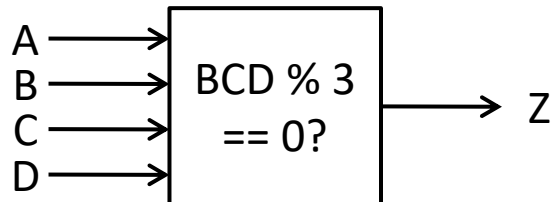

Decimal Digit	8-4-2-1 Code	ABCD	Z
0	0000	0000	1
1	0001	0001	0
2	0010	0010	0
3	0011	0011	1
4	0100	0100	0
5	0101	0101	0
6	0110	0110	1
7	0111	0111	0
8	1000	1000	0
9	1001	1001	1
		1010	X
		1011	X
		1100	X
		1101	X
		1110	X
		1111	X

Outline

- ❑ Conversion of English Sentences to Boolean Equations
- ❑ Combinational Logic Design Using a Truth Table
- ❑ Minterm and Maxterm Expansions
- ❑ General Minterm and Maxterm Expansions
- ❑ Incompletely Specified Functions
- ❑ Examples of Truth Table Construction
- ❑ **Design of Binary Adders and Subtractors**

1-Bit Half Adder (HA)

❑ Step 1: construct the truth table


X	Y	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

❑ Step 2: simplify the function

➤ $C = XY$

➤ $S = X'Y + XY' = X \oplus Y$

❑ Step 3: realize it

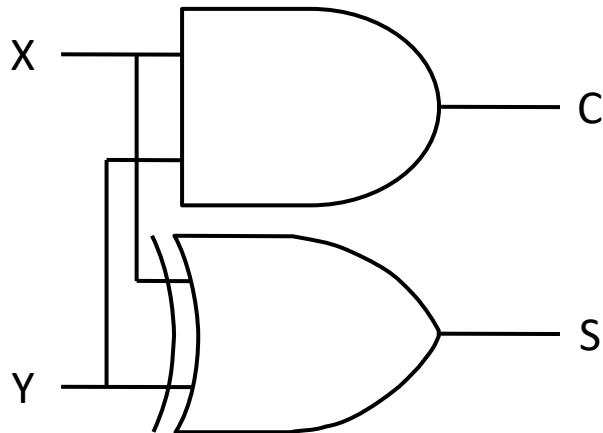

1-Bit Full Adder (FA)

Step 1: construct the truth table

Step 2: simplify the function

$$C_{out} = X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in}$$

$$= XY + XC_{in} + YC_{in}$$

$$S = X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in}$$

Step 3: realize it

X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



两个1进位


三个1进位

两个、一个1进位
和的值=1

三个1进位
和=1

是否有奇数个1

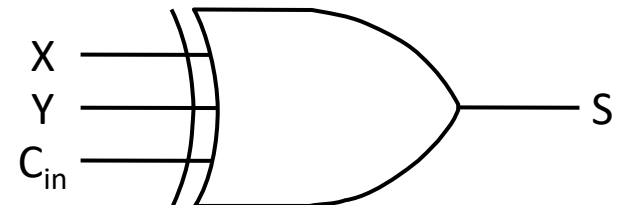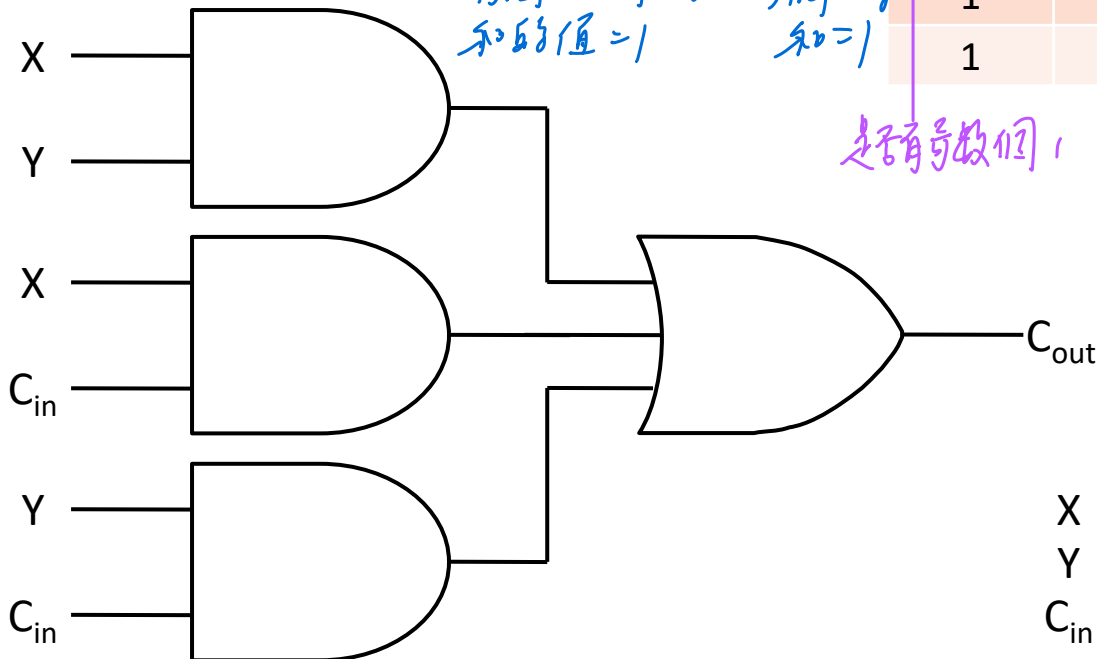


$$\begin{aligned} \text{Cont} &= \underline{X'Y C_m} + \underline{XY' C_m} + \underline{XY C_m'} + \underline{XY C_m} \\ &= \underline{Y C_m} + \underline{X(Y' C_m + Y C_m')} \\ &= Y C_m + X \end{aligned}$$

$$\begin{aligned} &Y C_m + X Y' C_m + X Y C_m' \\ &= Y(C_m + X C_m') \\ &= Y(C_m + X) \\ &= Y C_m + XY \end{aligned}$$

4-Bit Parallel Adder (1/3)

□ $A = (A_3A_2A_1A_0)$, $B = (B_3B_2B_1B_0)$


$$\begin{array}{r}
 \\
 \\
 \\
 \\
 \hline
 C_4 \leftarrow S_3 \leftarrow C_0 \\
 \text{carry-out} \text{carry-in}
 \end{array}$$

□ Example

$$\begin{array}{r}
 \\
 \\
 \\
 \\
 \hline
 1 \leftarrow 1 \leftarrow 0 \\
 \text{carries}
 \end{array}$$

□ How?

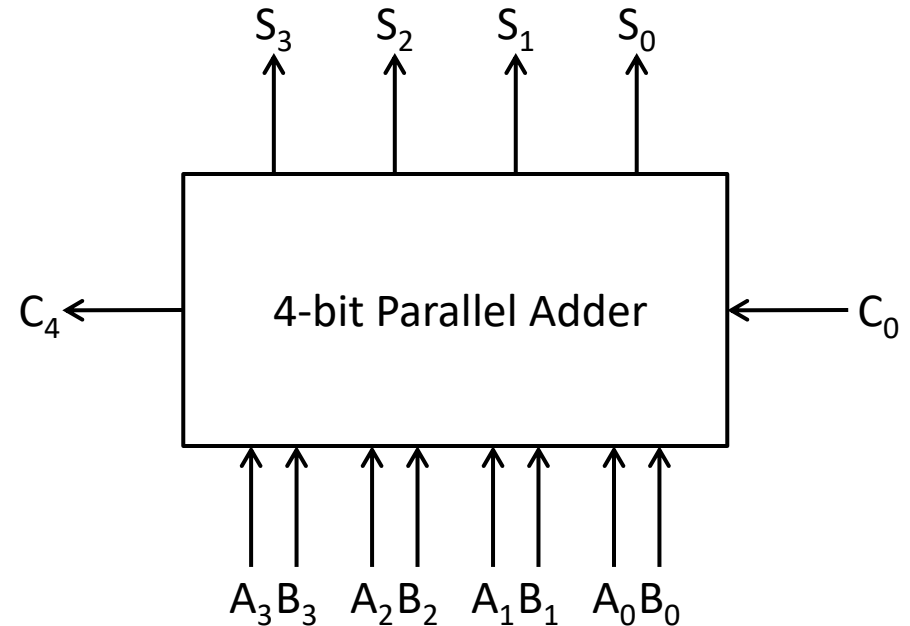- Step 1: construct the truth table
- ...



4-Bit Parallel Adder (2/3)

把 4 bit adder 拆成 4 个 1 bit 的 subcomponent

即 full adder

□ Decompose the 4 bit adder into four modules

➤ Each module adds two bits and a carry → use full adder

□ Extend to negative numbers

➤ Consider 1's complement

- Add just as if all numbers are positive
- Add the carry out back to the rightmost bit


➤ How to detect overflow?

- Check the sign
 - (+) + (+) becomes (-)
 - (-) + (-) becomes (+)

Case 1	Case 2	Case 3	Case 4	Case 5	Case 6
+3 0011 +4 0100 <hr/> +7 0111	+5 0101 +6 0110 <hr/> 1011	+5 0101 -6 1001 <hr/> -1 1110	-5 1010 +6 0110 <hr/> +1 (1) 0000 <div style="text-align: right;">1</div> <hr/> <div style="text-align: right;">0001</div>	-3 1100 -4 1011 <hr/> -7 (1) 0111 <div style="text-align: right;">1</div> <hr/> <div style="text-align: right;">1000</div>	-5 1010 -6 1001 <hr/> (1) 0011 <div style="text-align: right;">1</div> <hr/> <div style="text-align: right;">0100</div>

正 + 正 变负 溢出 overflow

4-Bit Parallel Adder (3/3)

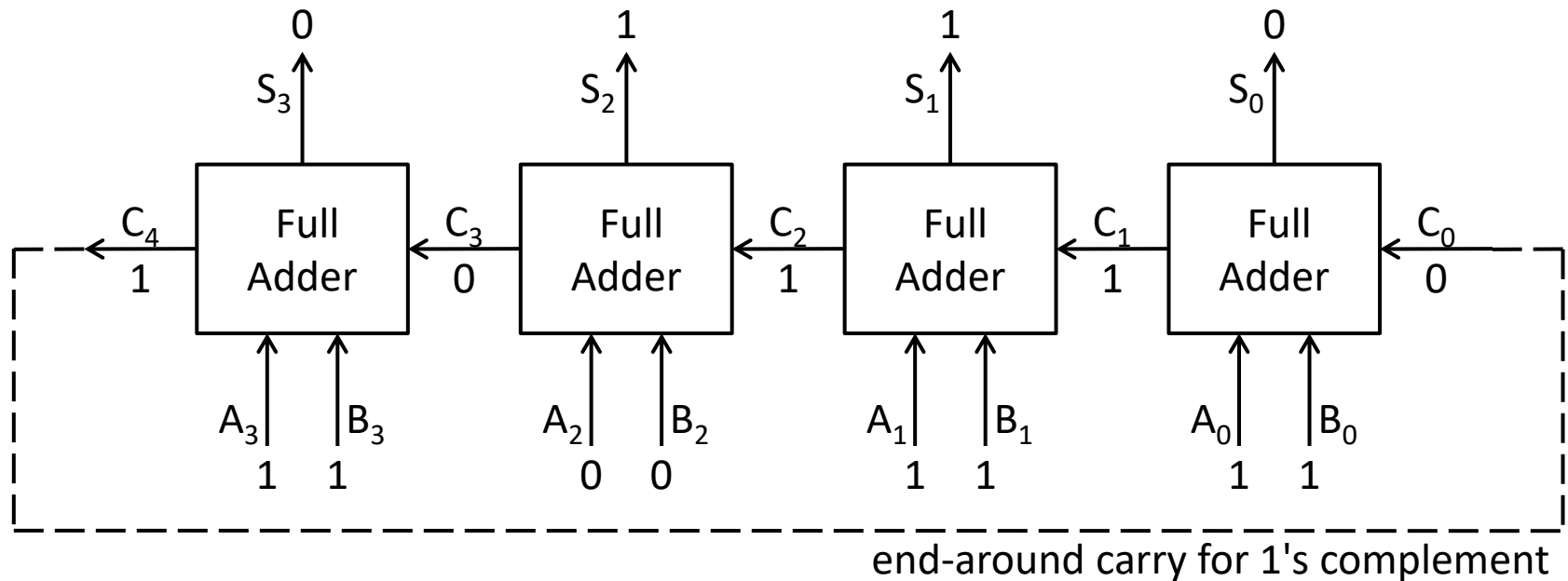

Overflow detection?

➤ $V = \overline{A_3} \overline{B_3} S_3 + \overline{A_3} B_3 \overline{S_3}$ 3 → 检查最前面的 bit

➤ Why?

↓
 $\overline{A_3} \overline{B_3} \rightarrow$ 正+正
 $S_3 \rightarrow$ 负

↓
 $A_3 B_3 \rightarrow$ 负+负
 $S_3' \rightarrow$ 正

Binary Subtractor (1/2)


所有位反過來再加1

❑ Consider $A - B = A + (-B)$ in 2's complement

➤ $A - B = A + (-B) = A + B^* = A + \bar{B} + 1$

➤ Convert B to 2's complement: inverse and then add 1


❑ Discard the carry from the sign bit

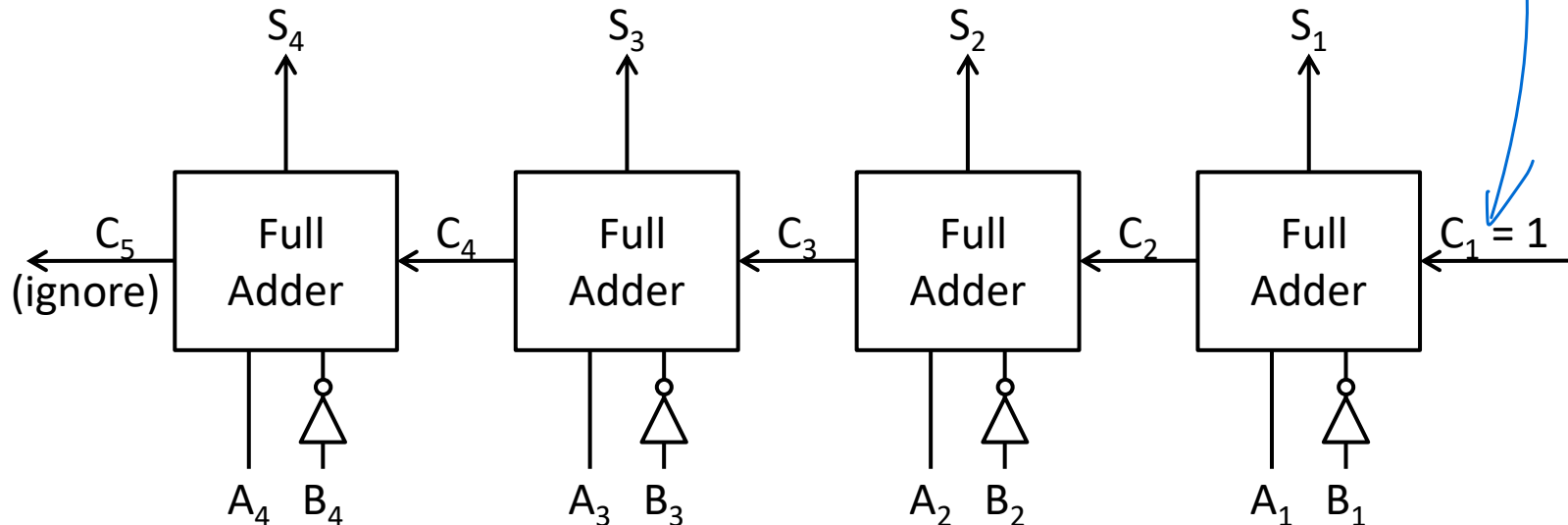

Binary Subtractor (2/2)

□ Or design a full subtractor

- $D = X - Y$: difference
- B : borrow

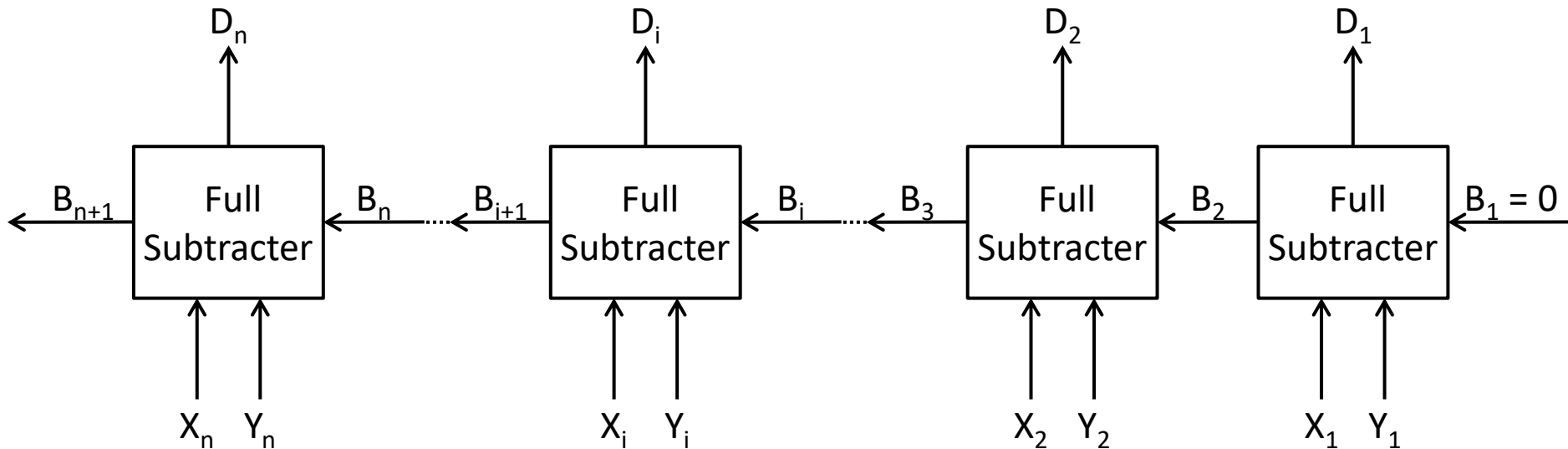

Q&A